

EECS 370 - Lecture 11

Single & Multi-Cycle Data Path




Announcements

- P2
 - Two parts: part a is due **next Thursday**
- HW 2
 - Posted on website, due next **Fri**
- Lab due Wed @ 11:55 pm
- Midterm exam after break **Thu 6-8 pm**
 - Sample exams on website
 - You can bring 1 sheet (double sided is fine) of notes
 - We will provide LC2K encodings + ARM cheat sheet
 - Calculator that doesn't connect to internet is recommended


Single-Cycle Processor Design

- General-Purpose Processor Design
 - Fetch Instructions
 - Decode Instructions
 - Instructions are input to control ROM
 - ROM data controls movement of data
 - Incrementing PC, reading registers, ALU control
 - Clock drives it all
 - Single-cycle datapath: Each instruction completes in one clock cycle

LC2K Datapath Implementation

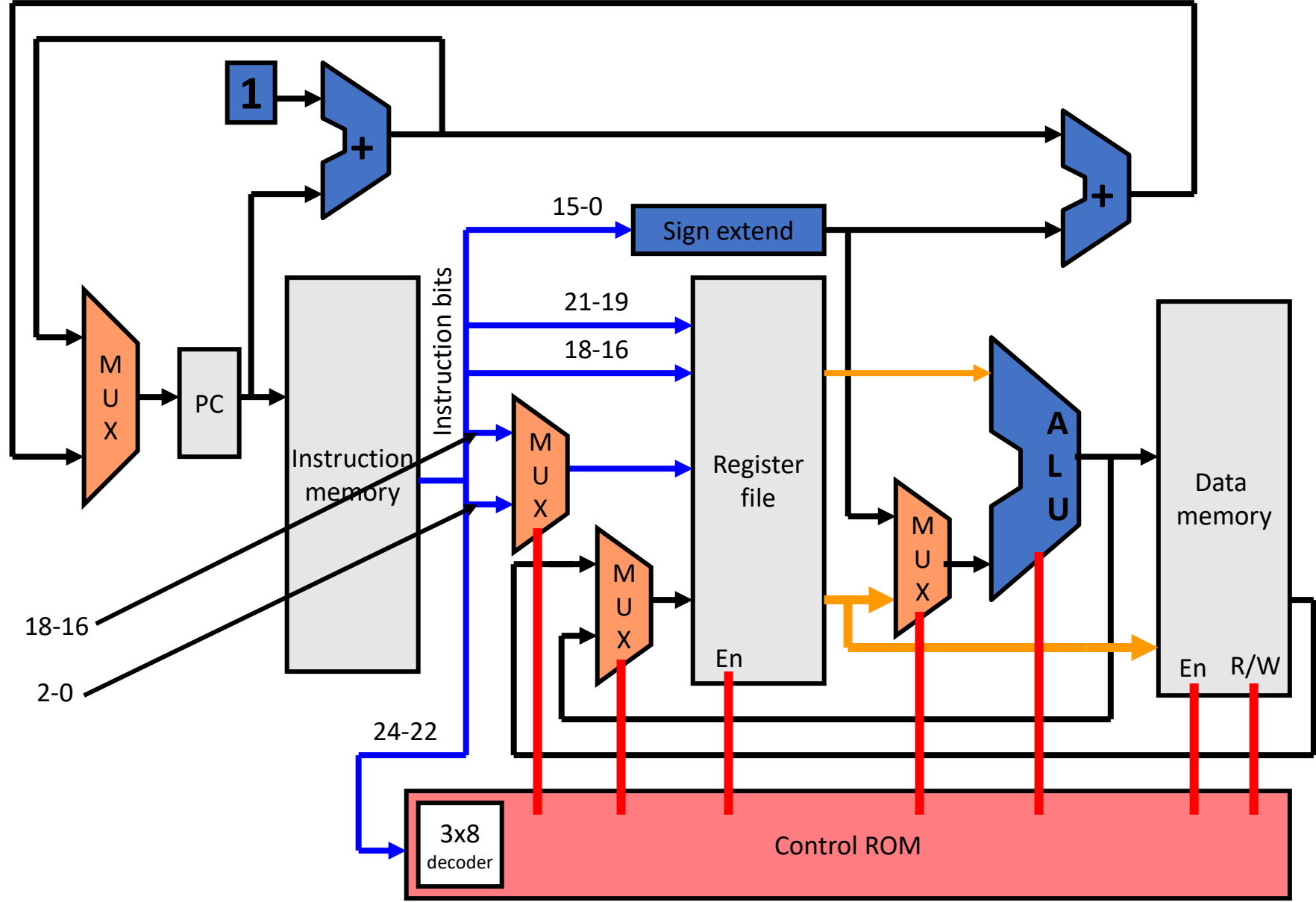


Building Blocks for the LC2K

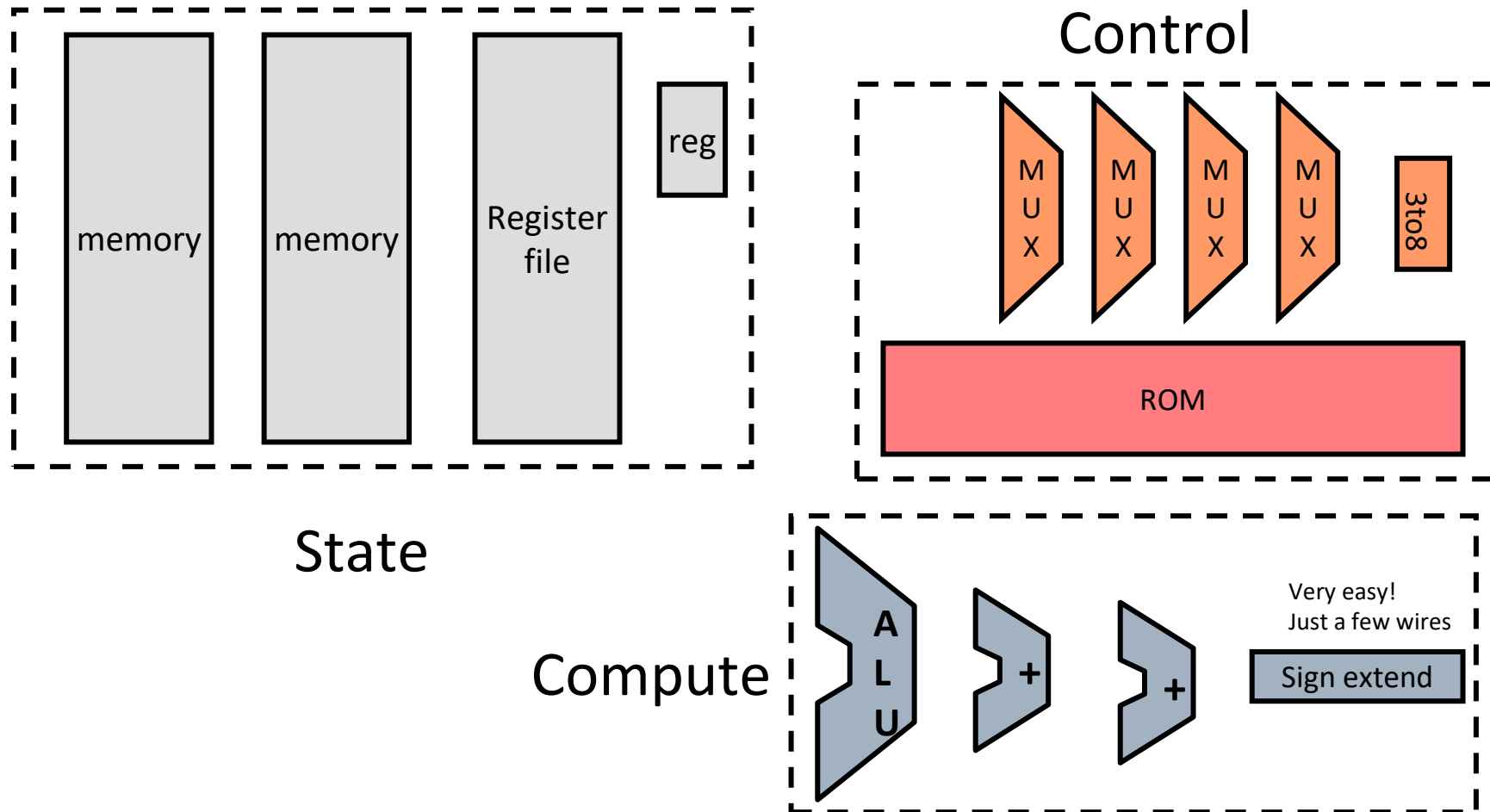

Here are the pieces, go build yourself a processor!


Control Building Blocks (1)

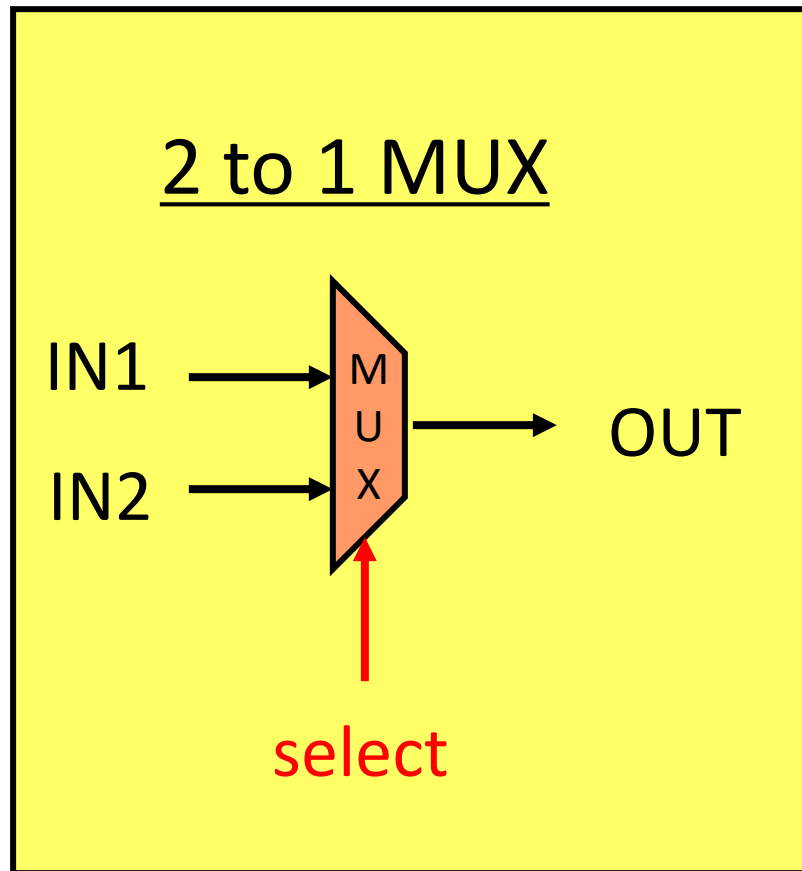

Connect one of the inputs to OUT based on the value of select

If (! select)
 OUT = IN1
Else
 OUT = IN2

Control Building Blocks (2)

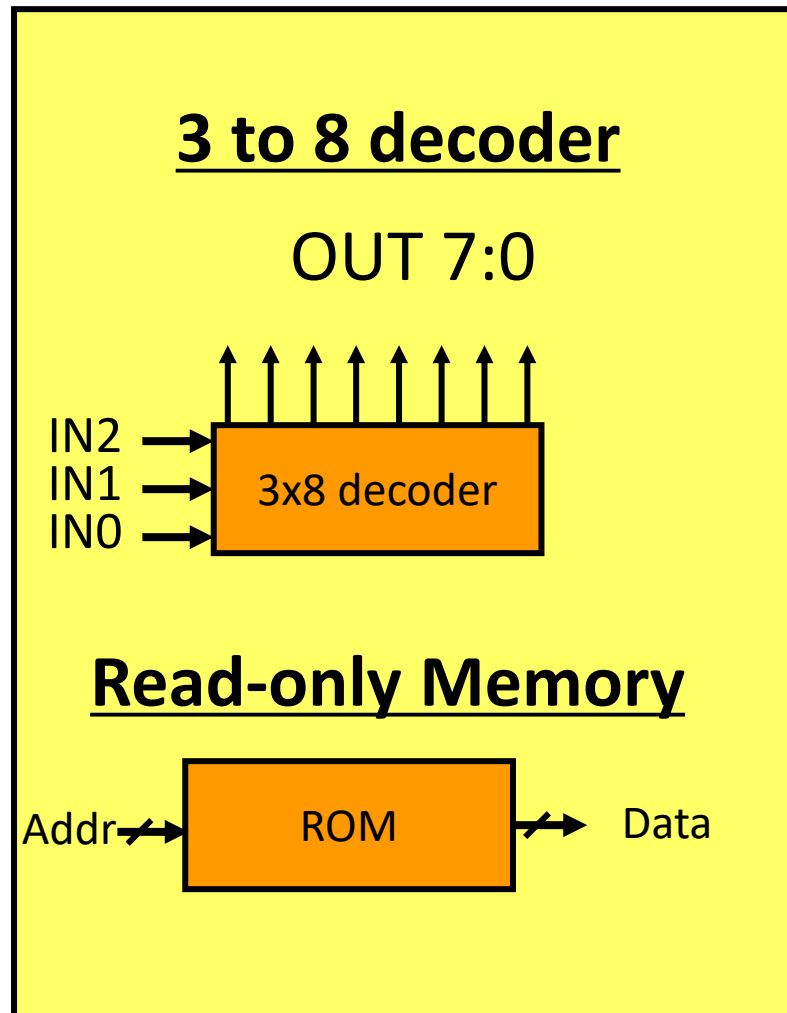


Decoder activates one of the output lines based on the input

IN	OUT
<u>210</u>	<u>76543210</u>
000	00000001
001	00000010
010	00000100
011	00001000
etc.	

ROM stores preset data in each location

- Give address, get data.

Compute Building Blocks (1)

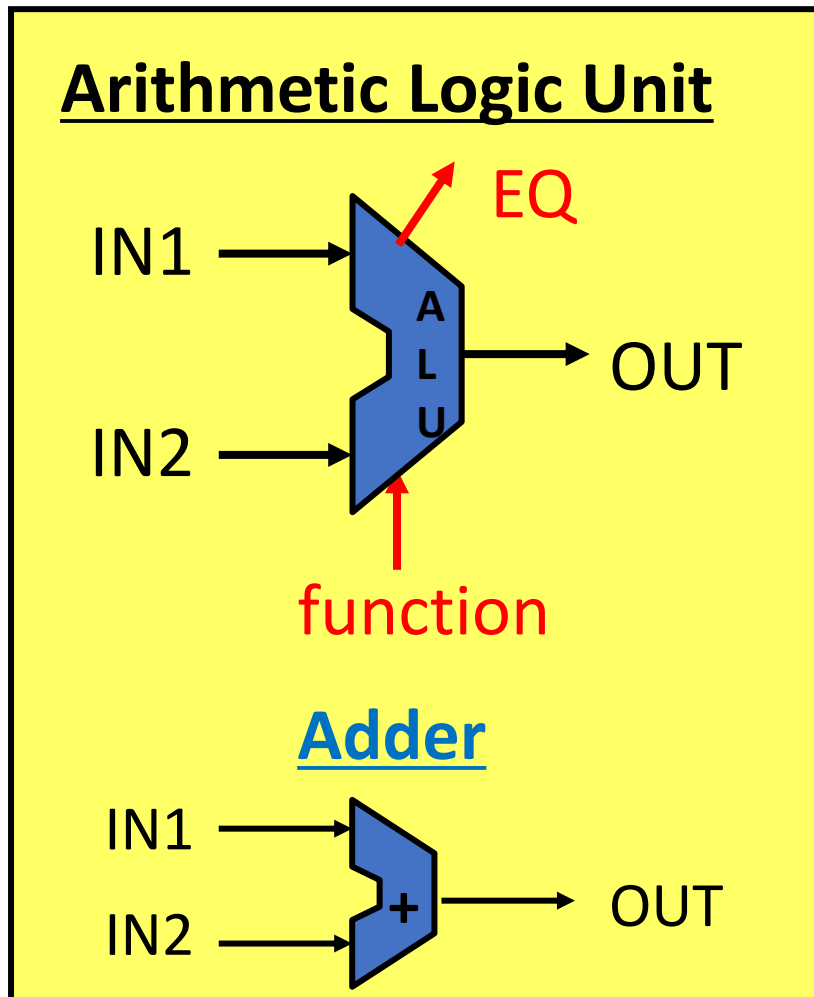

Perform basic arithmetic functions

$$\text{OUT} = f(\text{IN1}, \text{IN2})$$

$$\text{EQ} = (\text{IN1} == \text{IN2})$$

For LC2K:


f=0 is add

f=1 is nor

For other processors, there are many more functions.

Just adds

Compute Building Blocks (2)

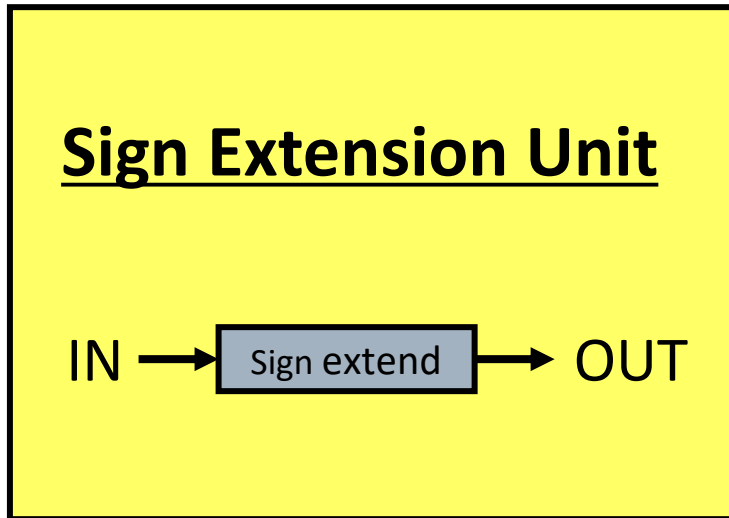

Sign extend (SE) input by replicating the MSB to width of output


$$\text{OUT}(31:0) = \text{SE}(\text{IN}(15:0))$$

$$\text{OUT}(31:16) = \text{IN}(15)$$

$$\text{OUT}(15:0) = \text{IN}(15:0)$$

Useful when compute unit is wider than data

State Building Blocks (1)

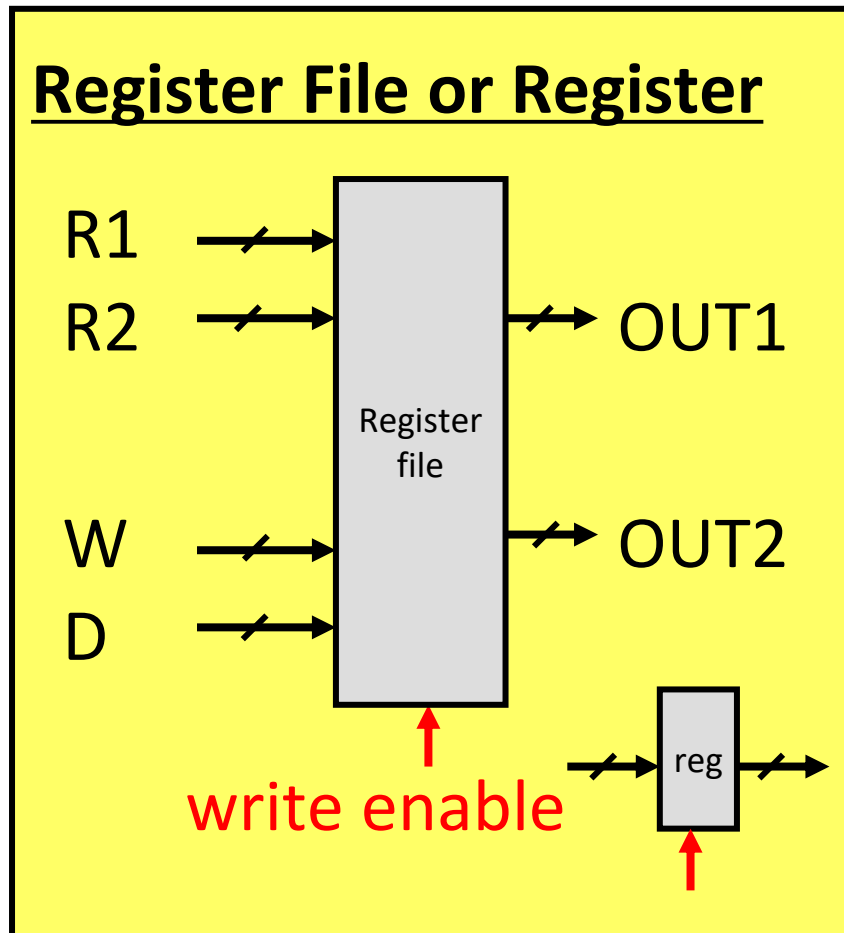

Small/fast memory to store temporary values

n entries (LC2 = 8)

r read ports (LC2 = 2)

w write ports (LC2 = 1)


* R_i specifies register number to read

* W specifies register number to write

* D specifies data to write

Poll: How many bits are R_i and W in LC2K?

State Building Blocks (2)

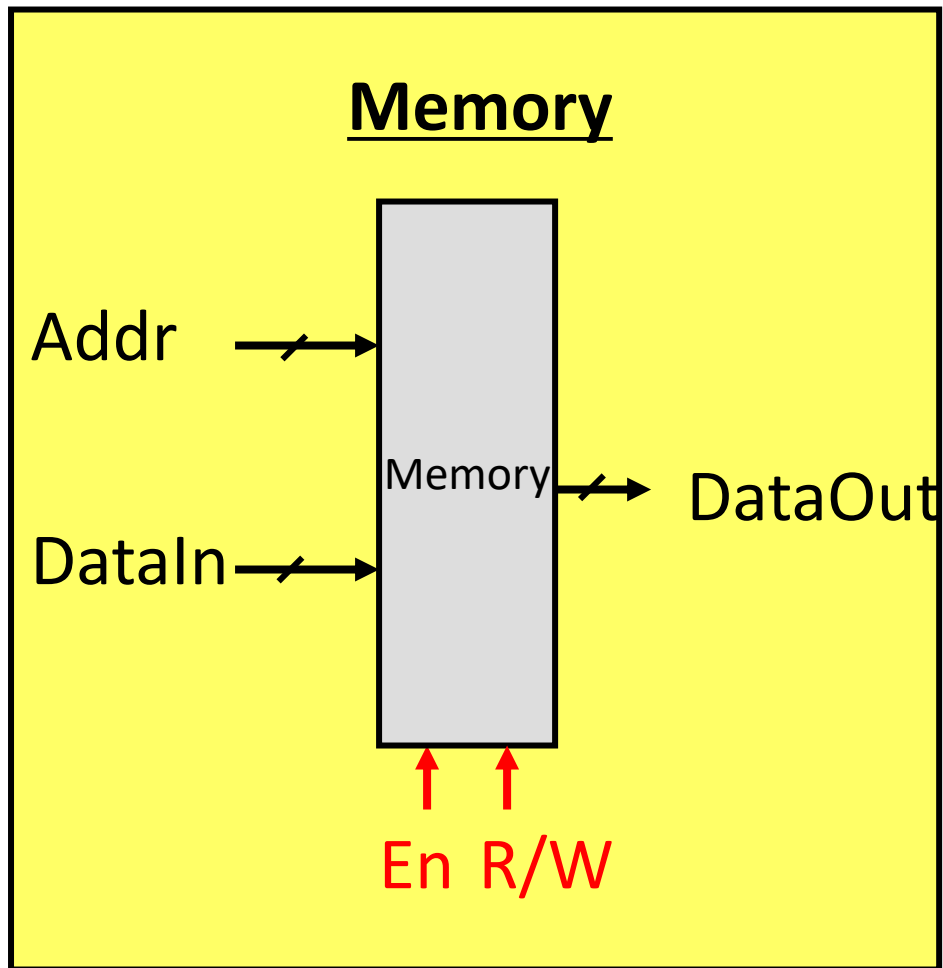


Slower storage structure to hold large amounts of stuff.

Use 2 memories for LC2K


- * Instructions
- * Data
- * 65,536 total words

Recap: LC2K Instruction Formats

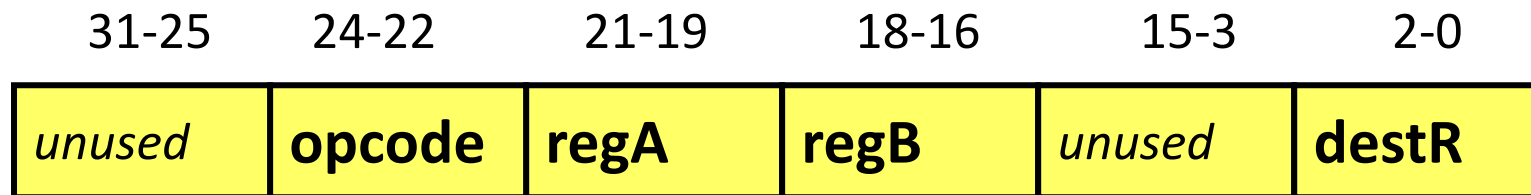
- Tells you which bit positions mean what
- R type instructions (add '000', nor '001')



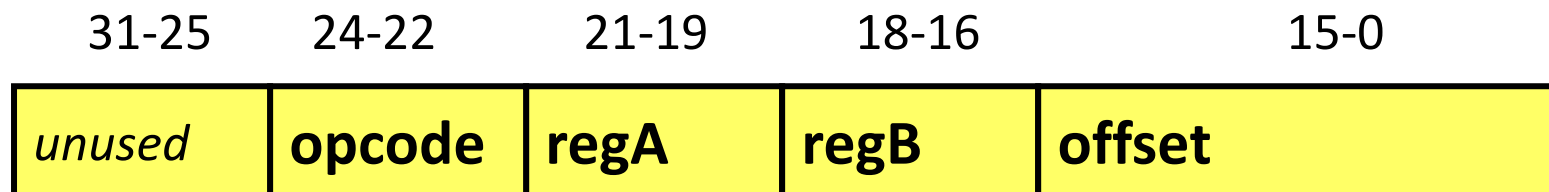
- I type instructions (lw '010', sw '011', beq '100')



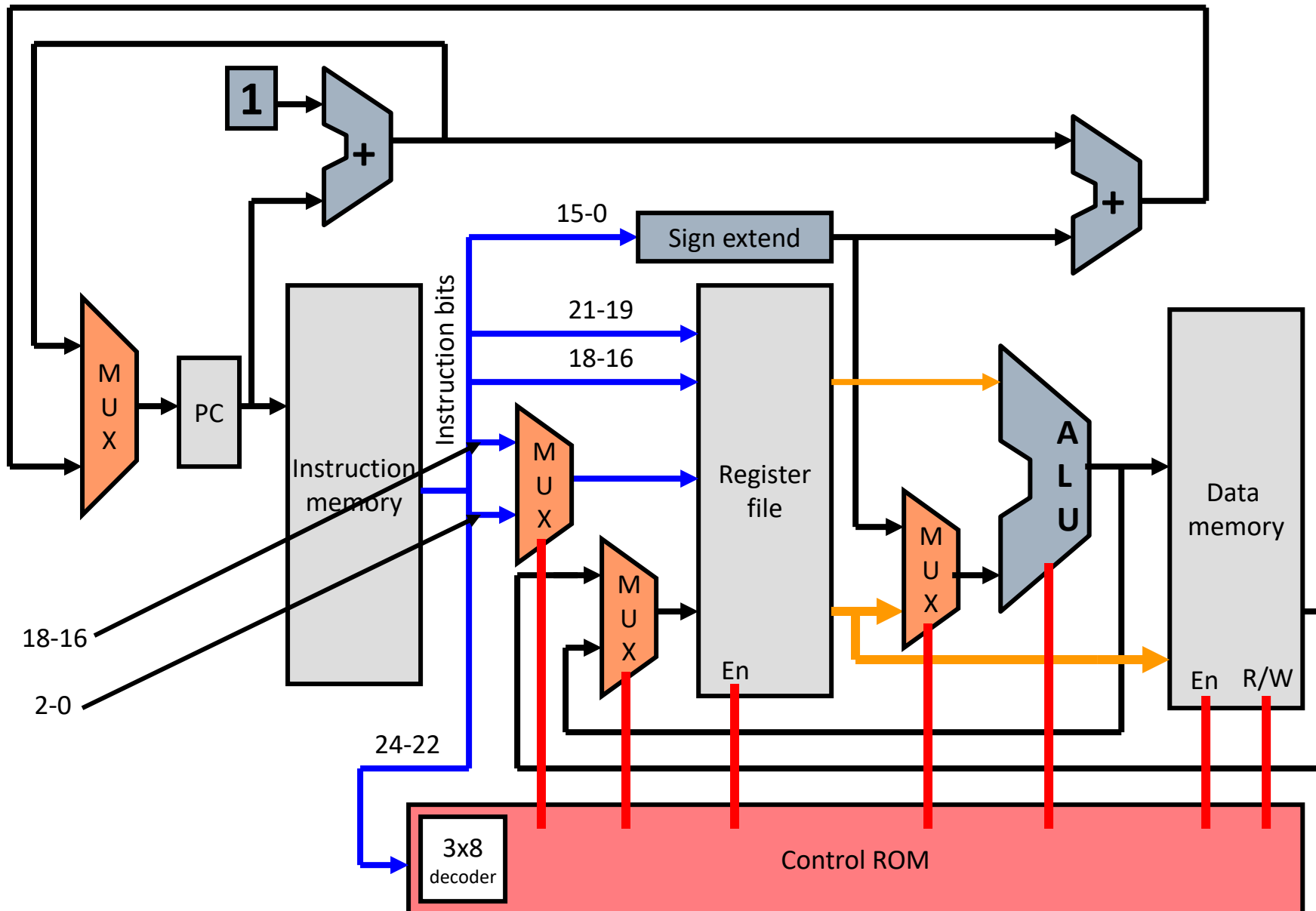
LC2K Single-Cycle Datapath Implementation



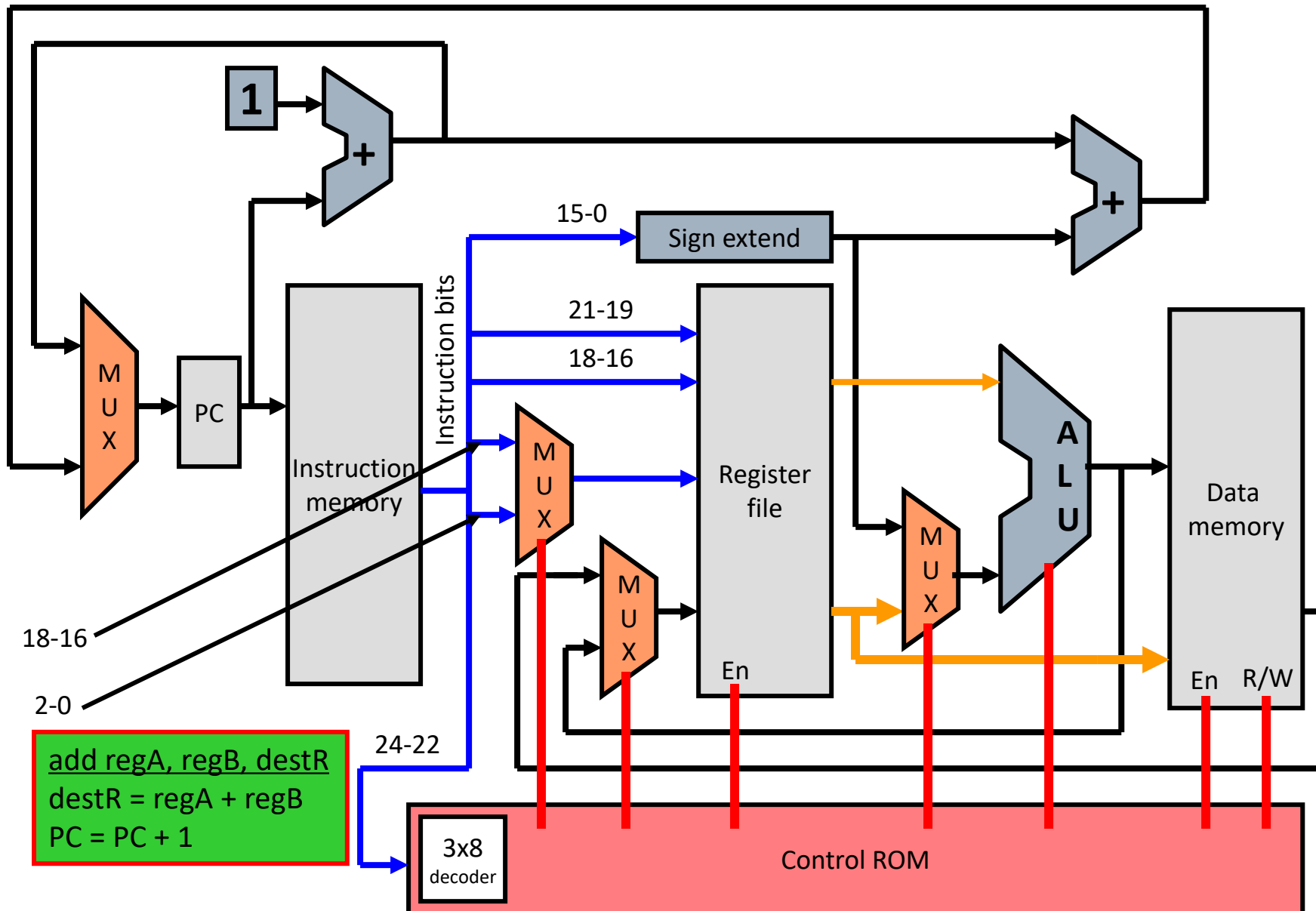Executing an **ADD** Instruction on LC2K Datapath




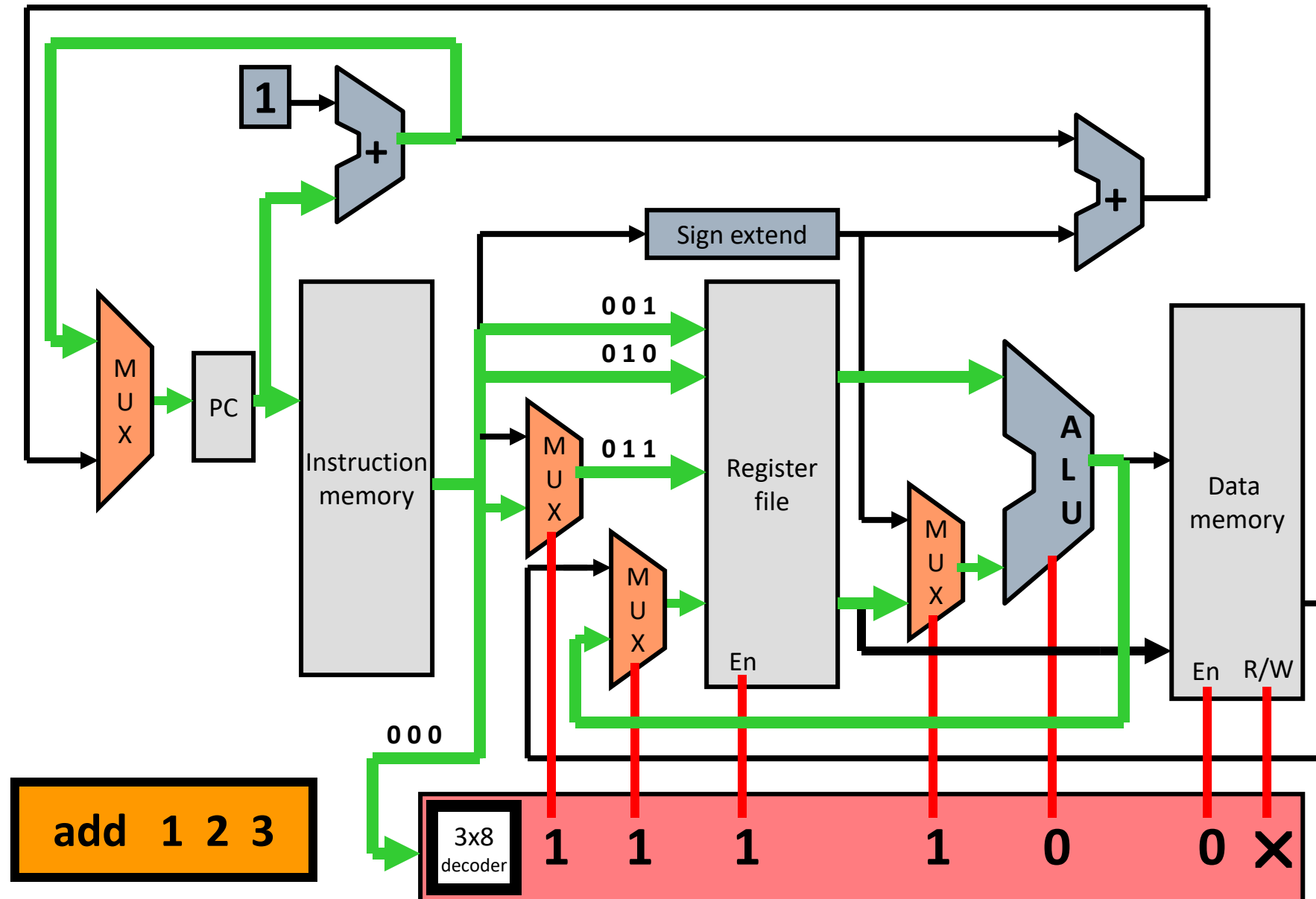Executing an **ADD** Instruction on LC2K Datapath




Poll: Which control bits need to be different from ADD?

Executing a **NOR** Instruction

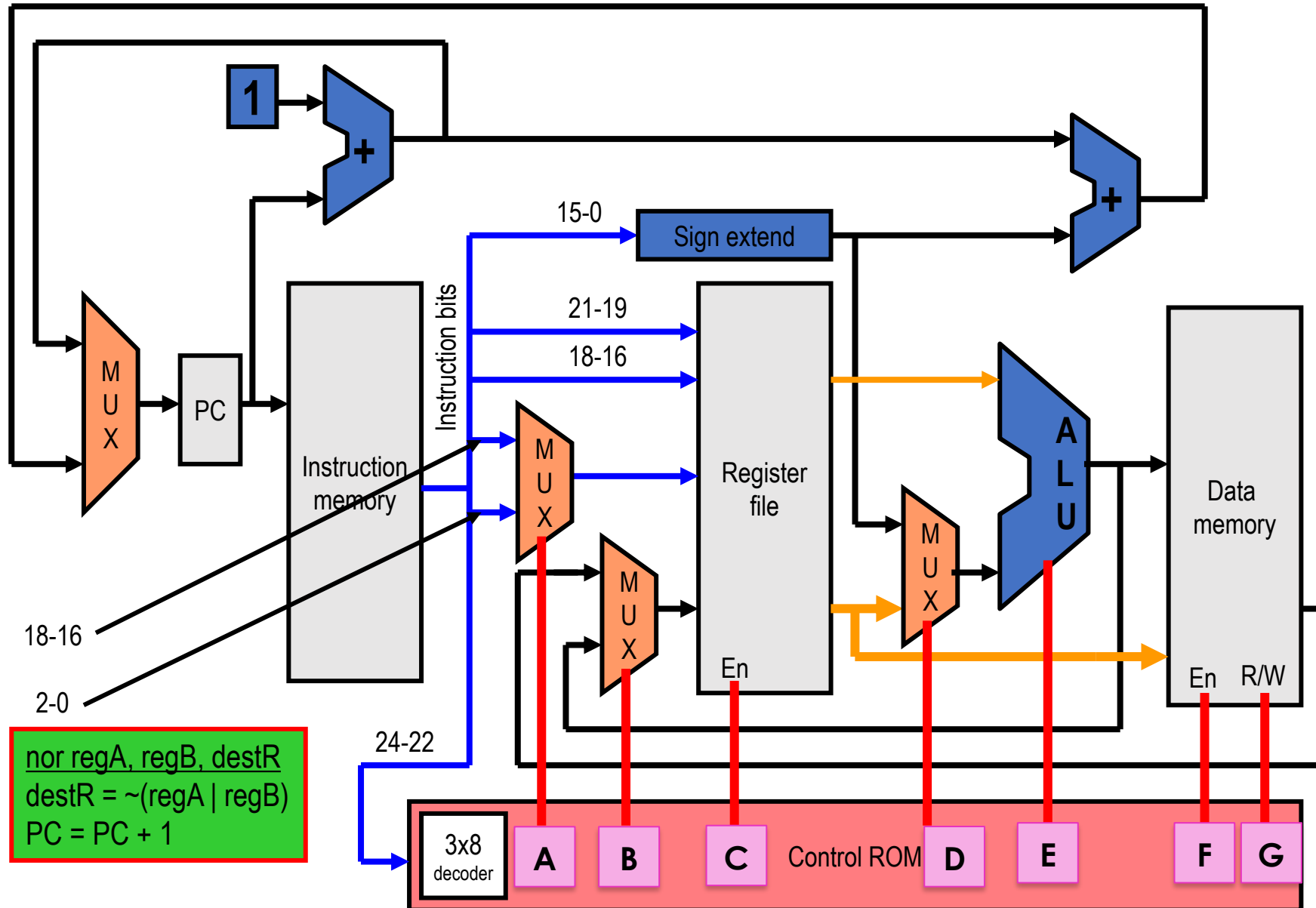


Executing a **NOR** Instruction

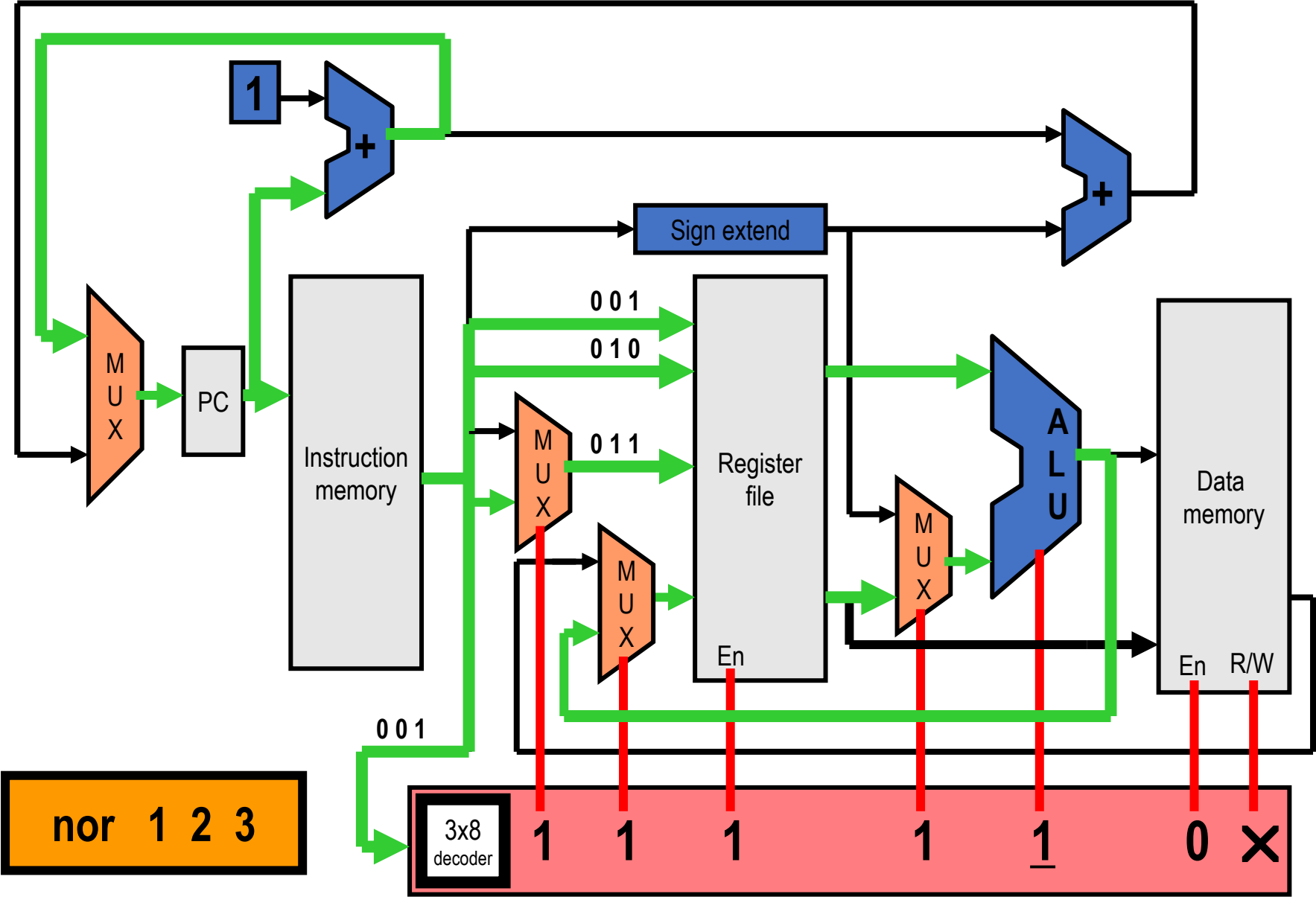


Executing a **LW** Instruction


31-25	24-22	21-19	18-16	15-0
unused	opcode	regA	regB	offset

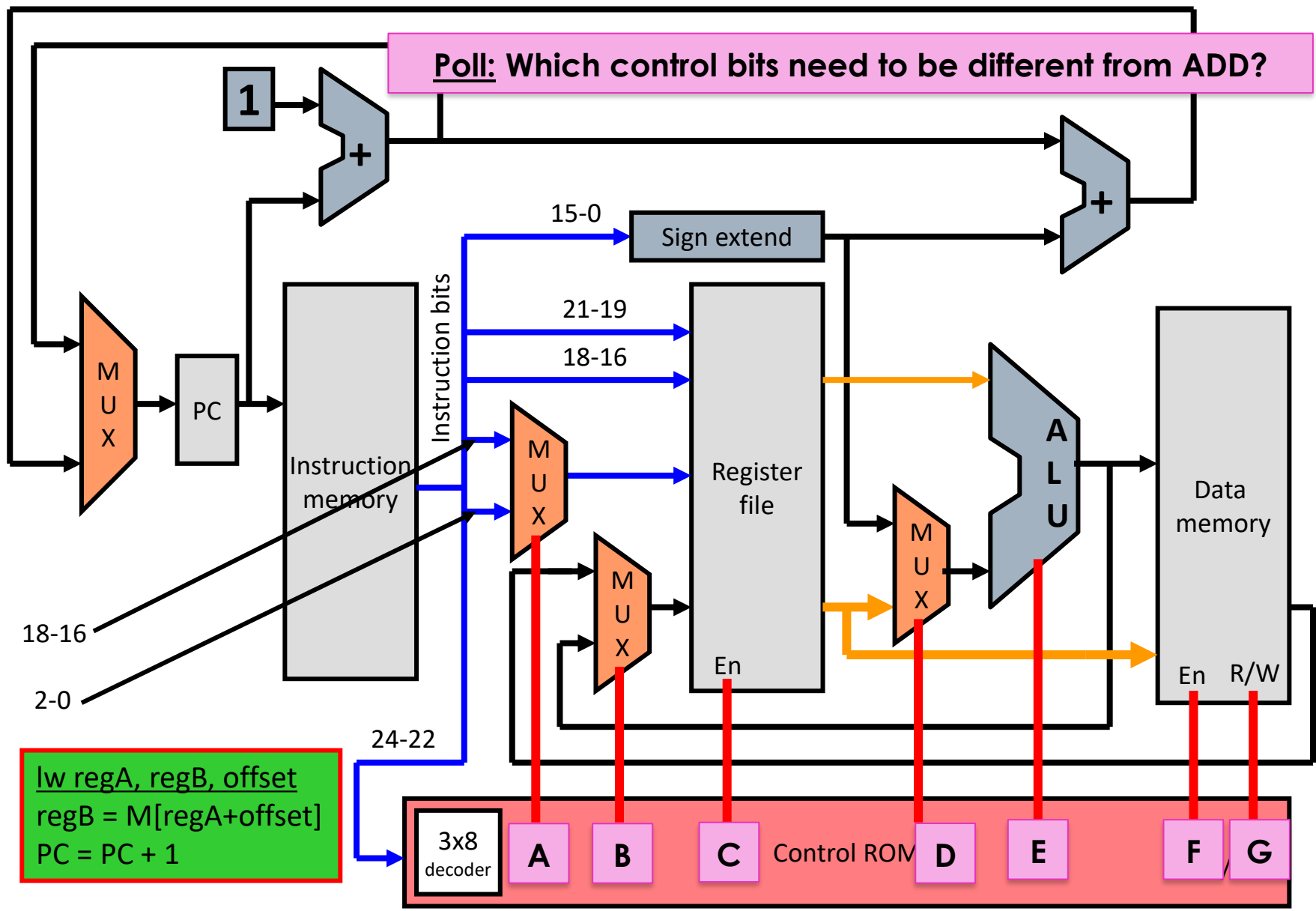


Executing a **LW** Instruction

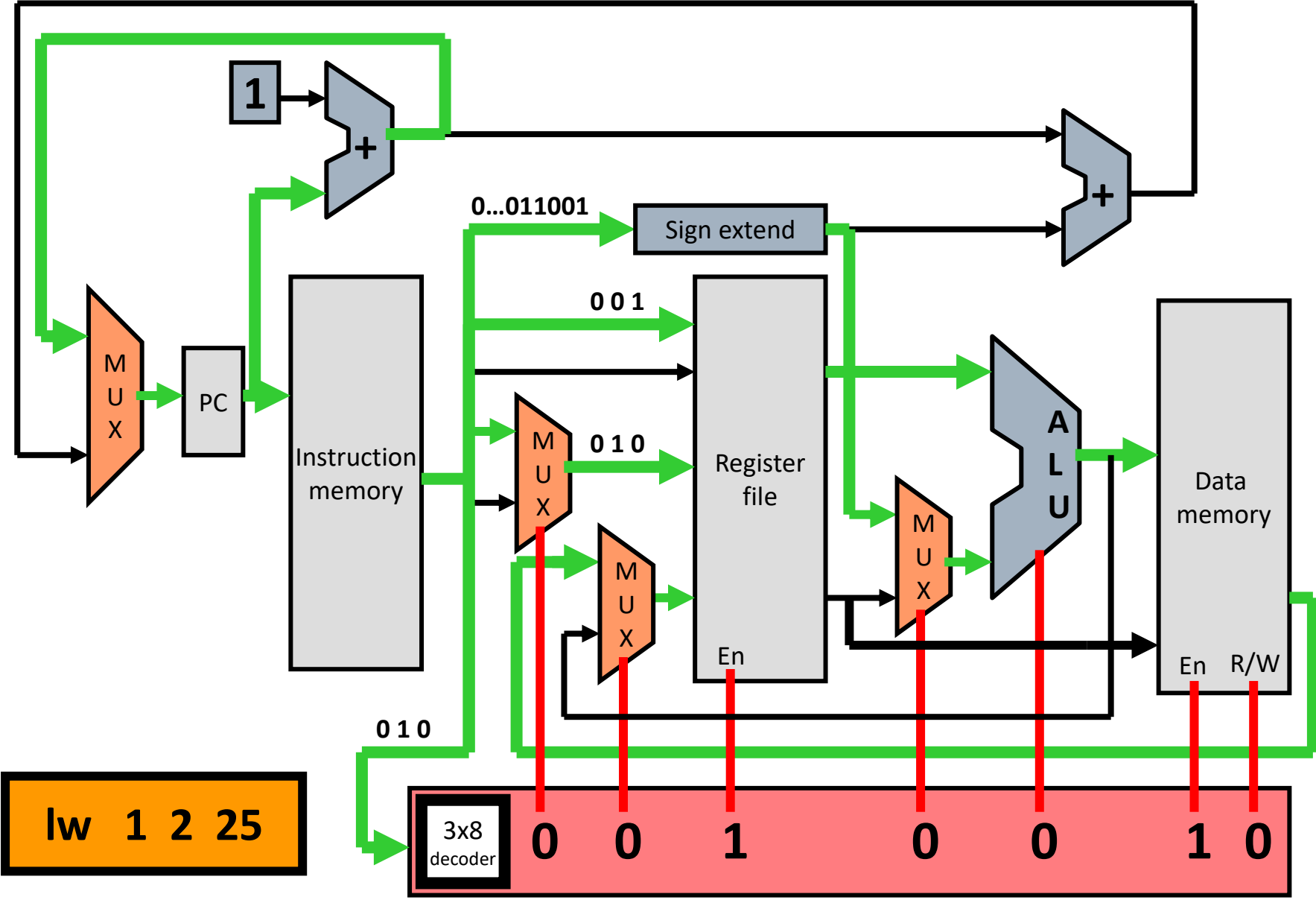


Executing a **SW** Instruction

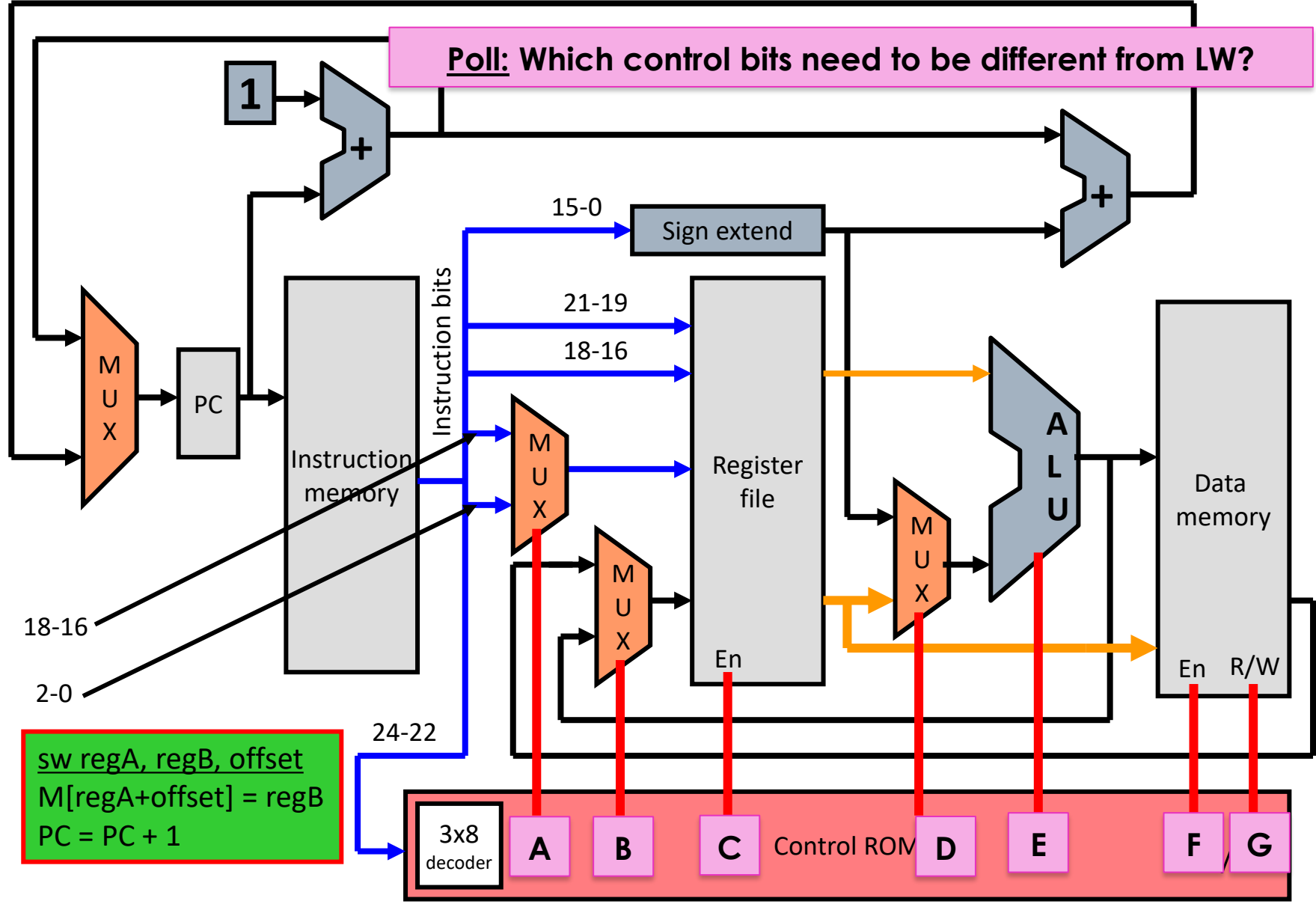


Executing a **SW** Instruction

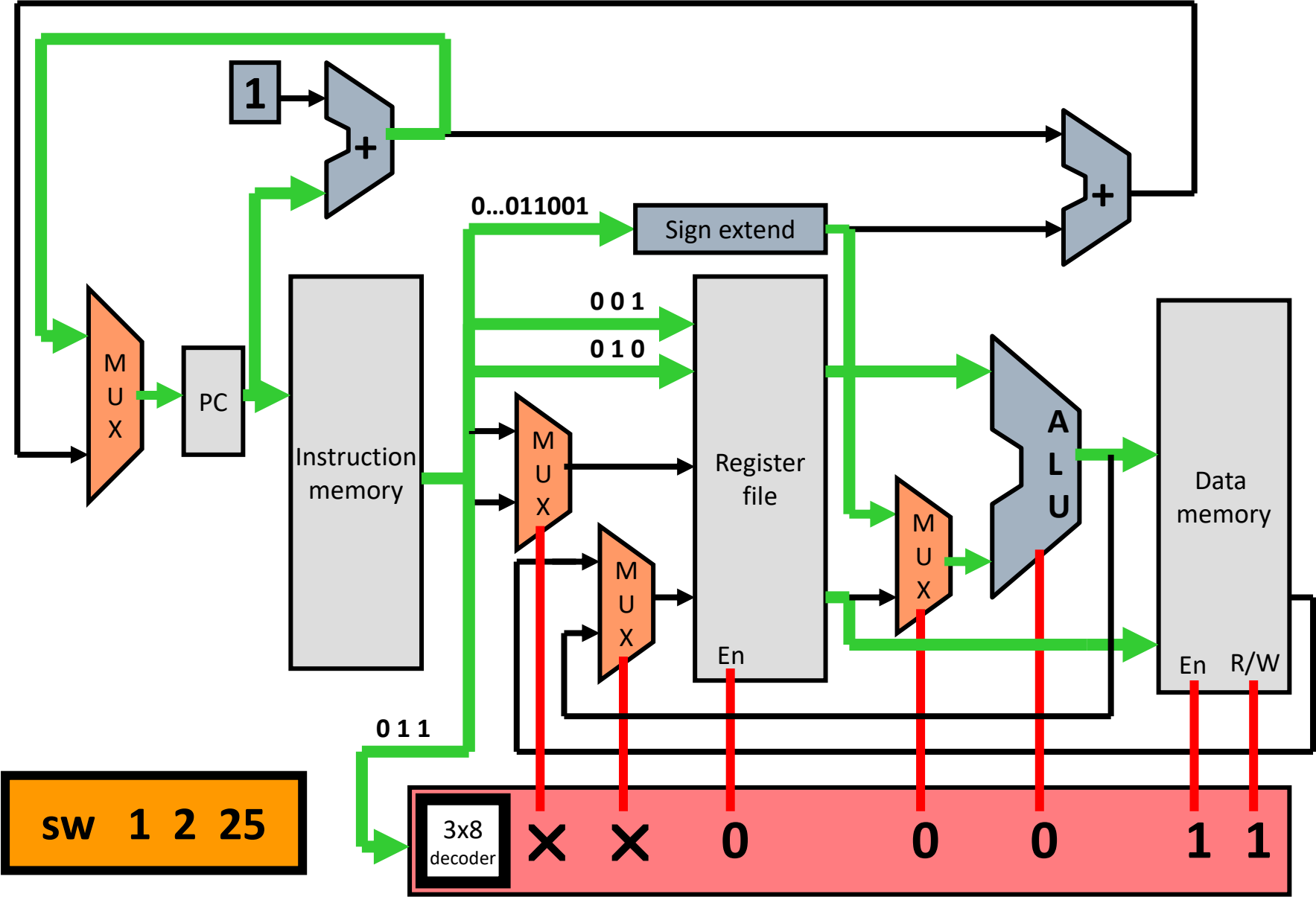


Executing a **BEQ** Instruction

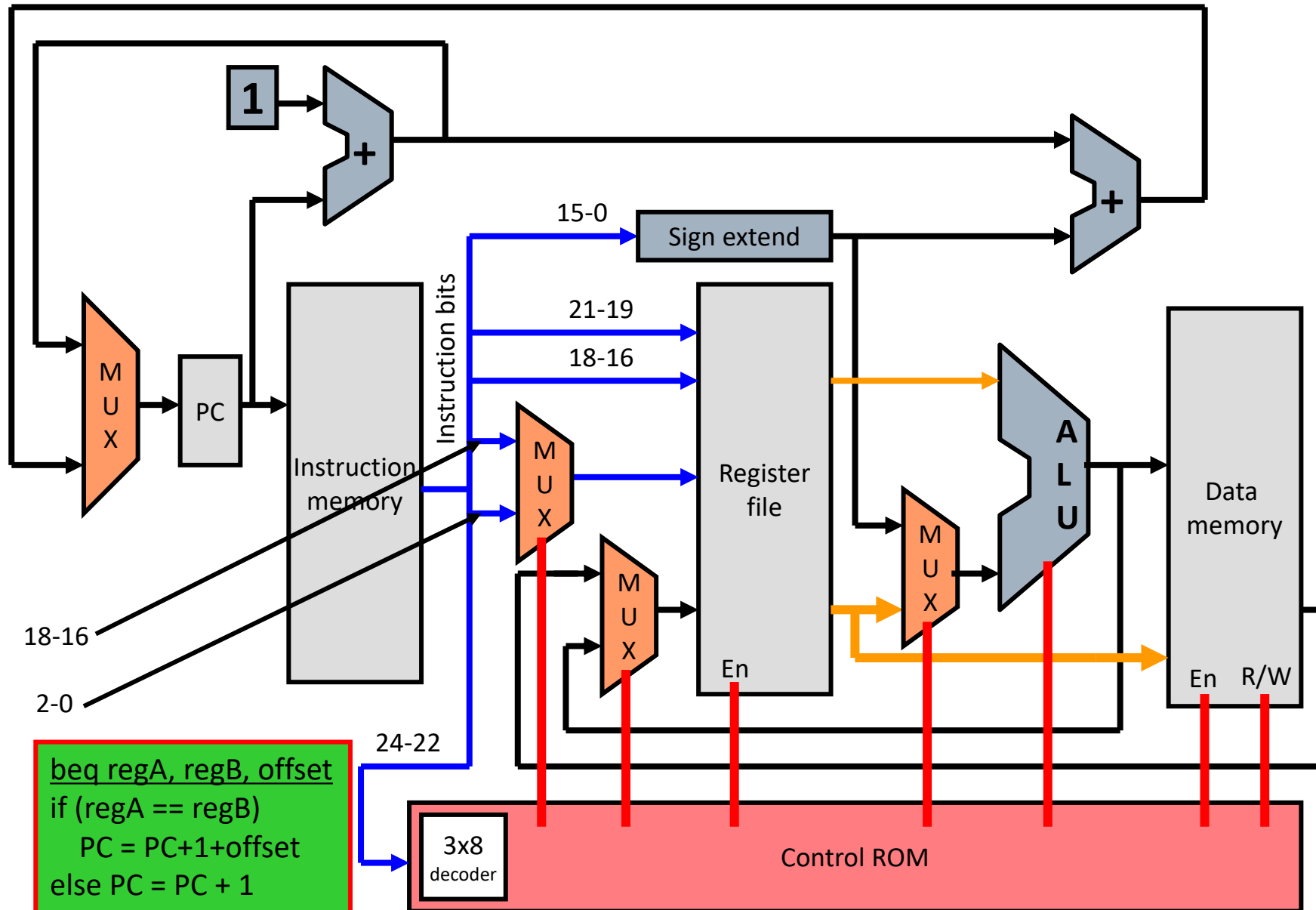

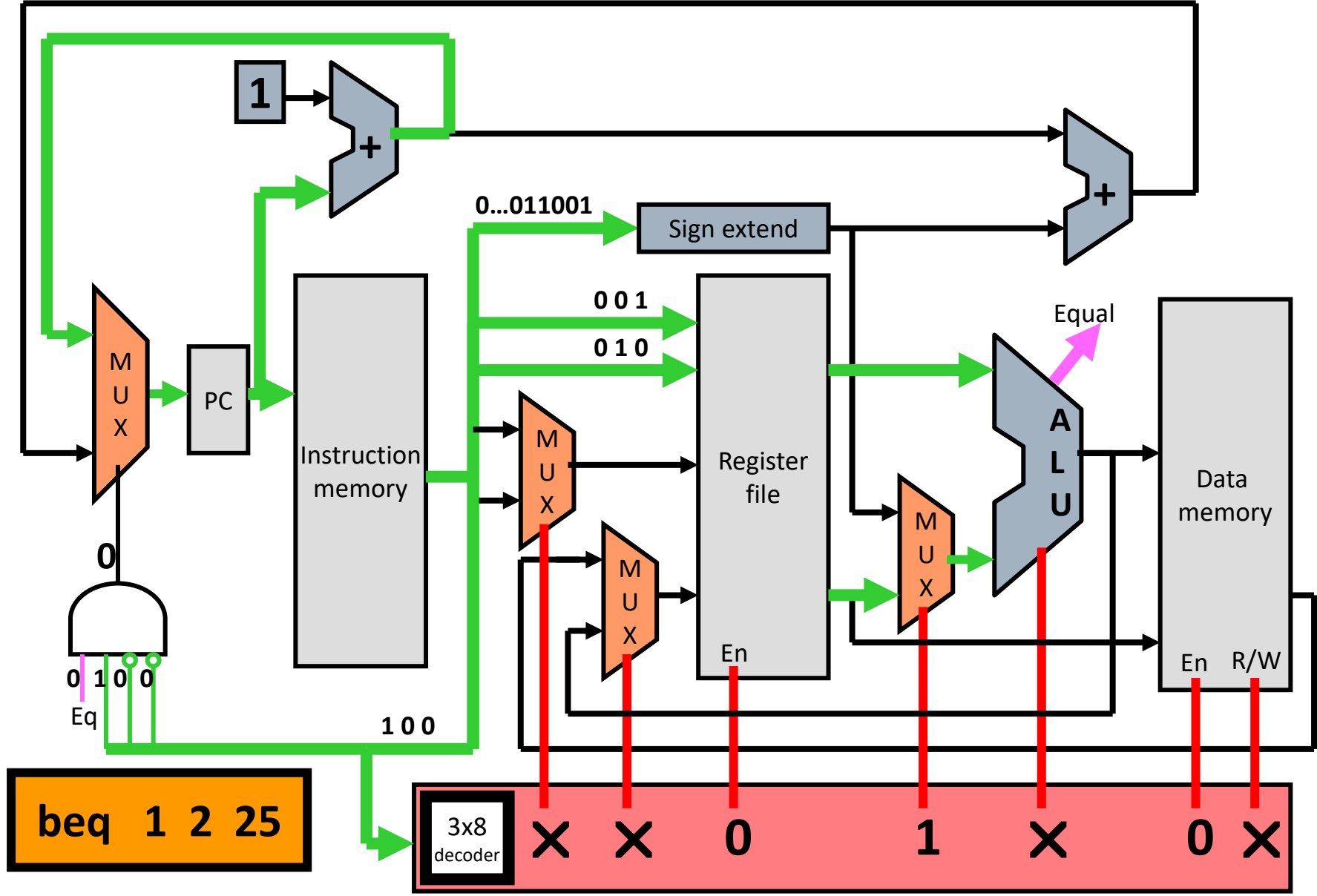Executing “not taken” **BEQ** Instruction on LC2K Datapath



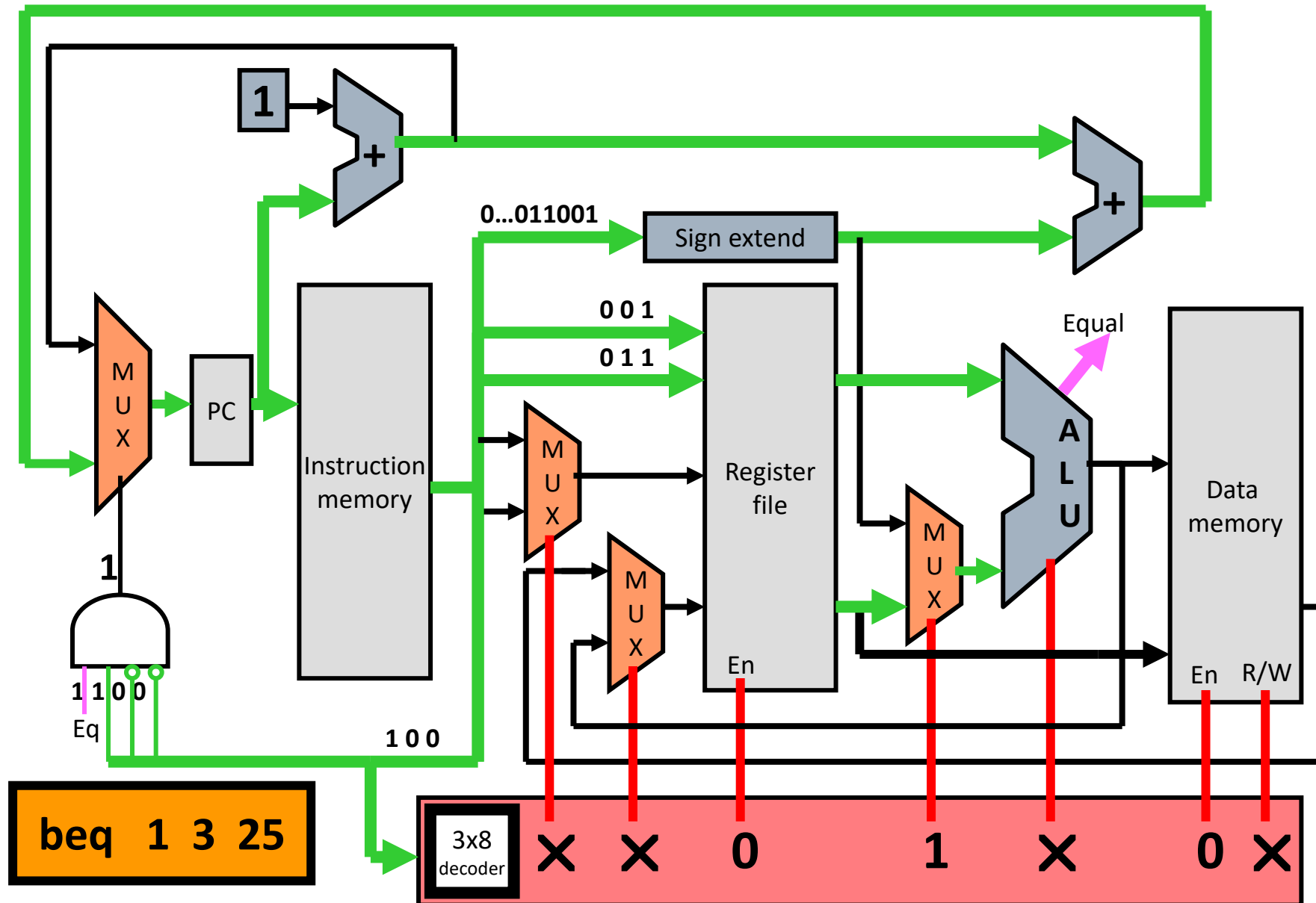
Executing a “taken” **BEQ** Instruction on LC2K Datapath




So Far, So Good

- Every architecture seems to have at least one "ugly" instruction
 - Something that doesn't elegantly fit in with the hardware we've already included
- For LC2K, that ugly instruction is JALR
 - It doesn't fine into our nice clean datapath
- To implement JALR we need to:
 - Write $PC+1$ into regB
 - Move regA into PC
- Right now there is:
 - No path to write $PC+1$ into a register
 - No path to write a register to the PC


Executing a JALR Instruction

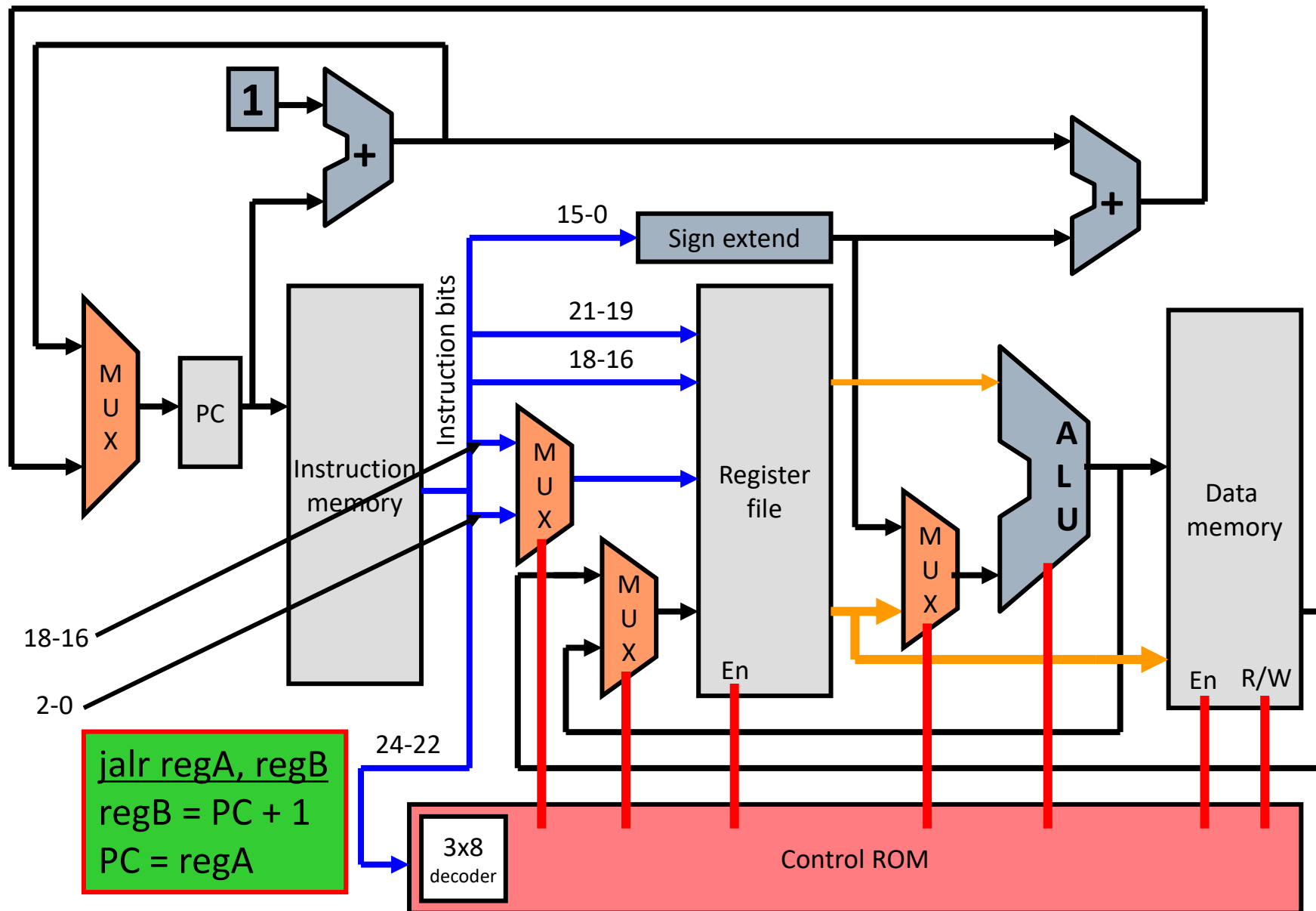


Executing a **JALR** Instruction

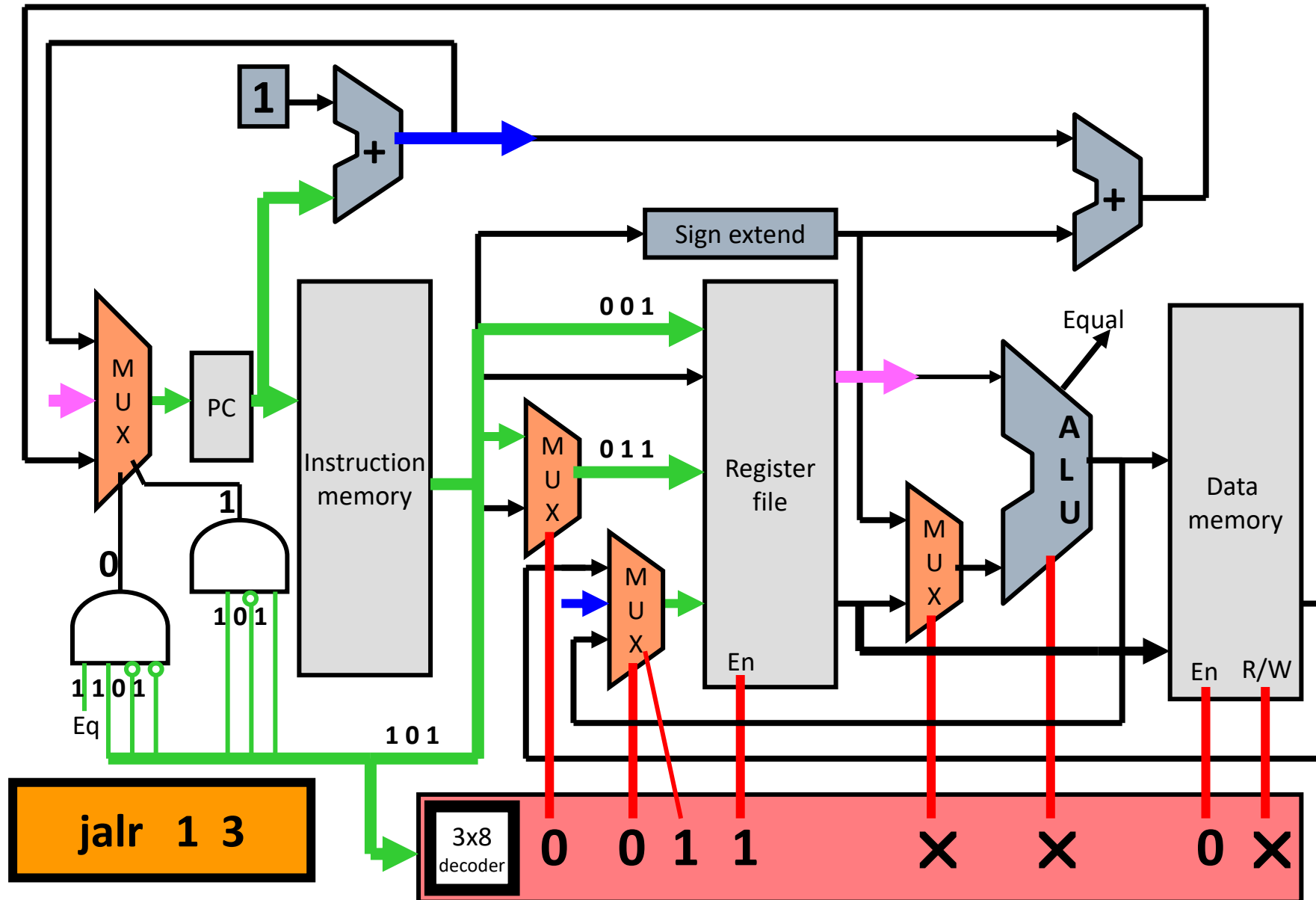

What if regA = regB for **JALR**?

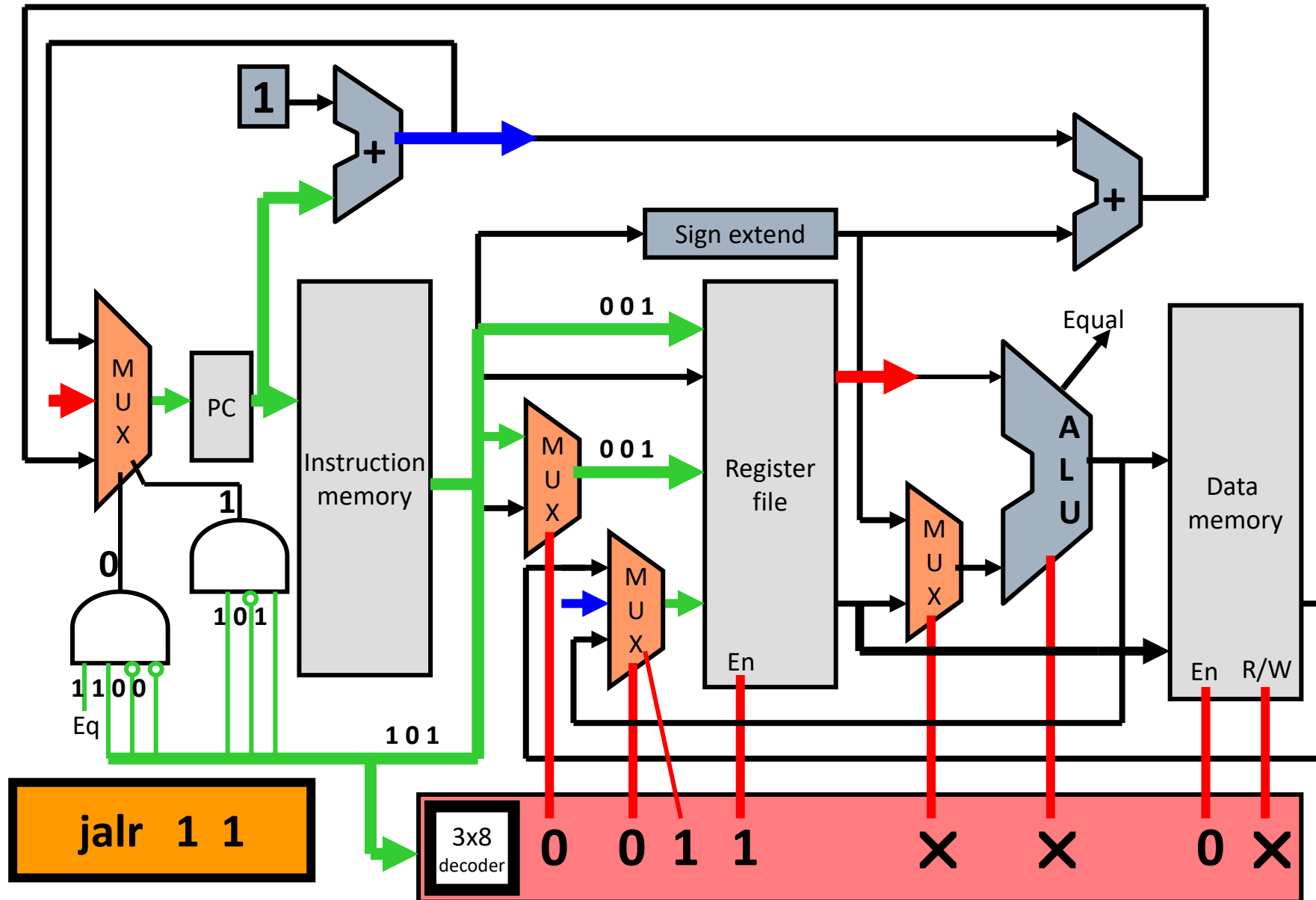

Changes for **JALR 1 1** Instruction

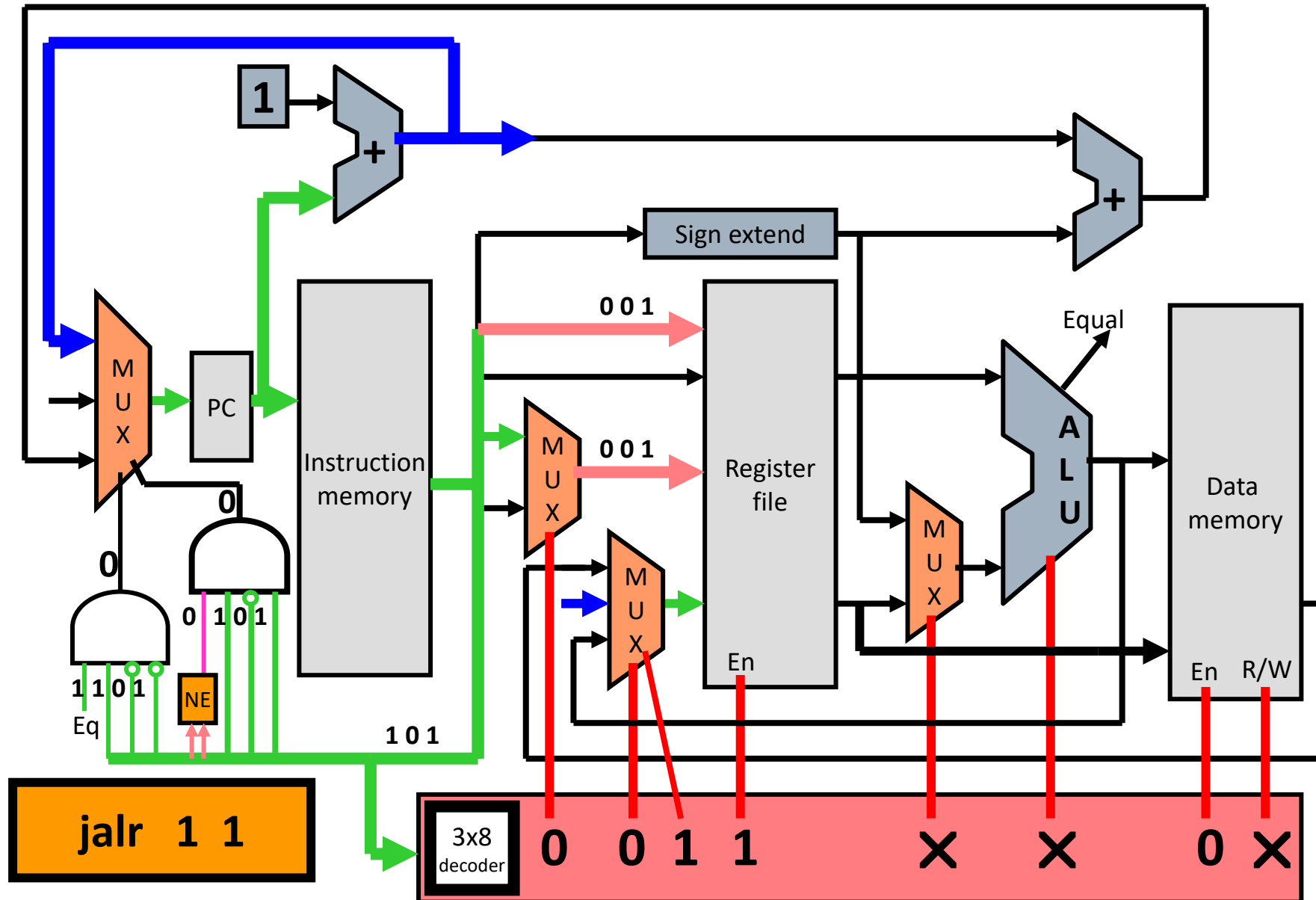

What's Wrong with Single-Cycle?

- **All instructions run at the speed of the slowest instruction.**
- Adding a long instruction can hurt performance
 - What if you wanted to include multiply?
- You cannot reuse any parts of the processor
 - We have 3 different adders to calculate $PC+1$, $PC+1+offset$ and the ALU
- No benefit in making the common case fast
 - Since every instruction runs at the slowest instruction speed
 - This is particularly important for loads as we will see later

What's Wrong with Single-Cycle?

- 1 ns – Register read/write time
- 2 ns – ALU/adder
- 2 ns – memory access
- 0 ns – MUX, PC access, sign extend, ROM

Poll: What is the latency of lw?

	Get Instr	read reg	ALU oper.	mem	write reg	
• add:	2ns	+ 1ns	+ 2ns		+ 1 ns	= 6 ns
• beq:	2ns	+ 1ns	+ 2ns			= 5 ns
• sw:	2ns	+ 1ns	+ 2ns	+ 2ns		= 7 ns
• lw:	2ns	+ 1ns	+ 2ns	+ 2ns	+ 1ns	= 8 ns

Computing Execution Time

Assume: 100 instructions executed

25% of instructions are loads,

10% of instructions are stores,

45% of instructions are adds, and

20% of instructions are branches.

Single-cycle execution:

??

Optimal execution:

??

Poll: What is the single-cycle execution time?

How fast could this run if we weren't limited by a single-clock period?

Computing Execution Time

Assume: 100 instructions executed

25% of instructions are loads,

10% of instructions are stores,

45% of instructions are adds, and

20% of instructions are branches.

Single-cycle execution:

$$100 * 8\text{ns} = \underline{\mathbf{800}} \text{ ns}$$


Optimal execution:

$$25*8\text{ns} + 10*7\text{ns} + 45*6\text{ns} + 20*5\text{ns} = \underline{\mathbf{640}} \text{ ns}$$


Multiple-Cycle Execution

- Each instruction takes multiple cycles to execute
 - Cycle time is reduced
 - Slower instructions take more cycles
 - Faster instructions take fewer cycles
 - We can start next instruction earlier, rather than just waiting
 - Can reuse datapath elements each cycle
- What is needed to make this work?
 - Since you are re-using elements for different purposes, you need more and/or wider MUXes.
 - You may need extra registers if you need to remember an output for 1 or more cycles.
 - Control is more complicated since you need to send new signals on each cycle.

LC2K Datapath – cycle groups

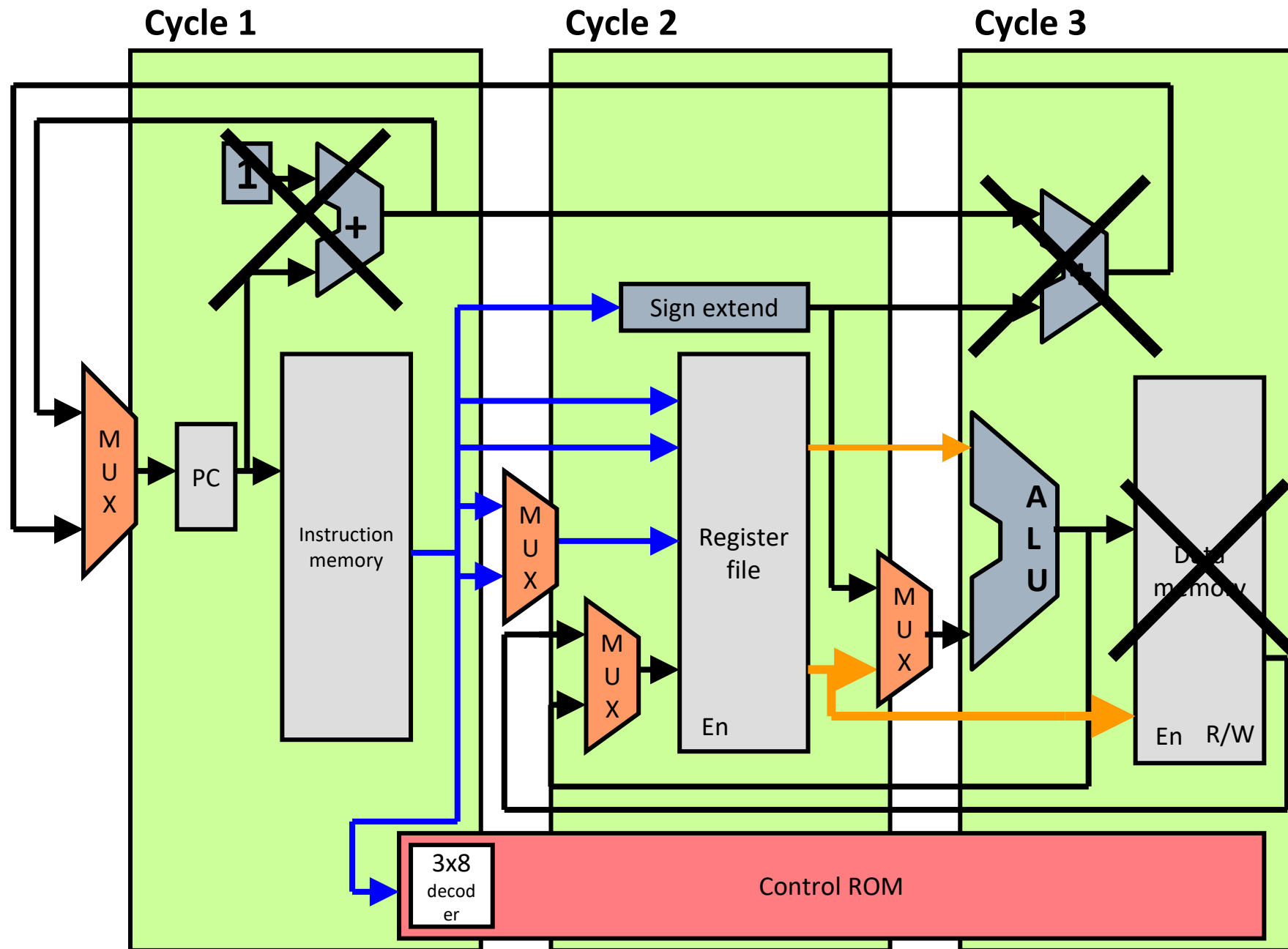


Multi-cycle LC2 Datapath

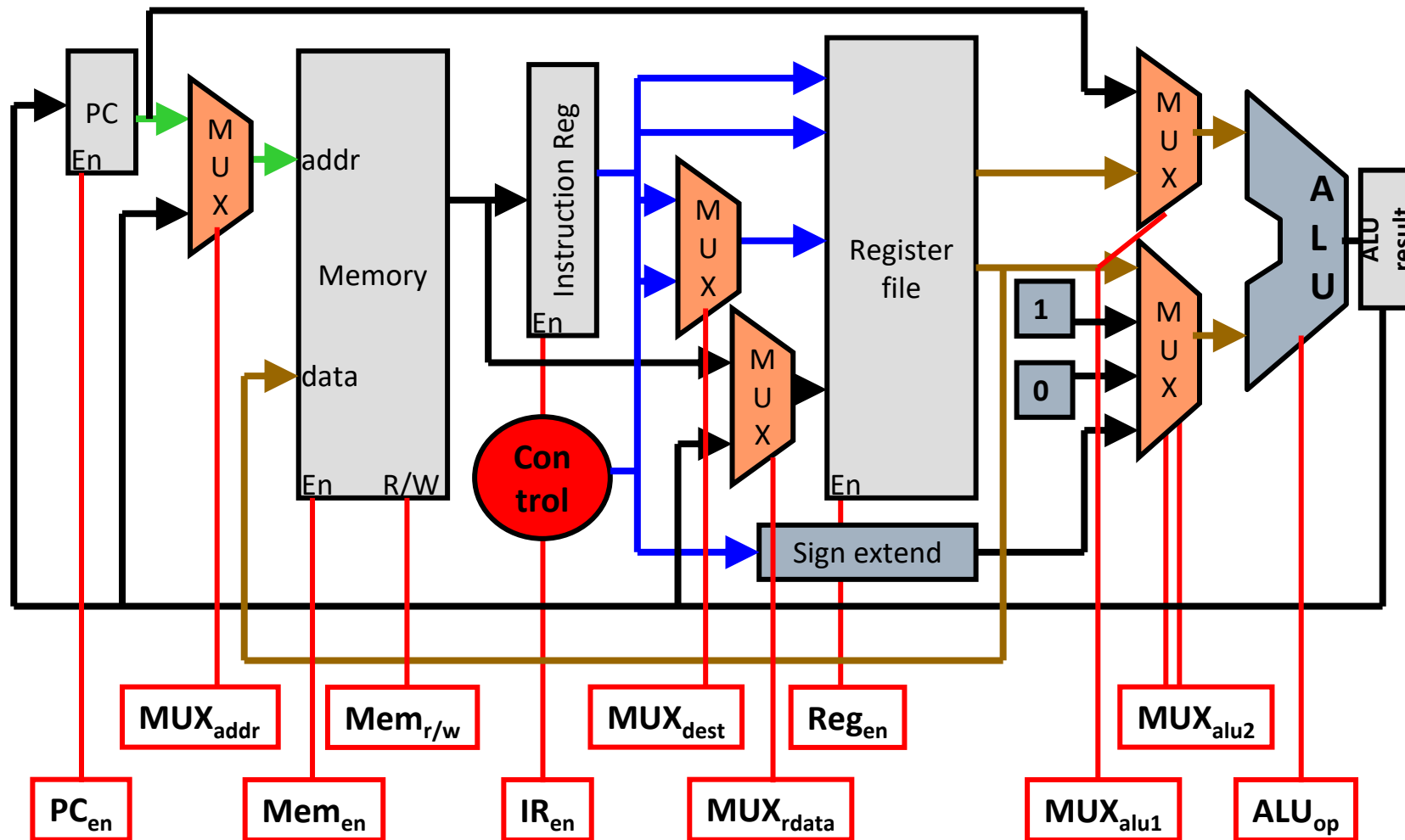

Each red signal comes from "Control"
(implemented via ROM as before)

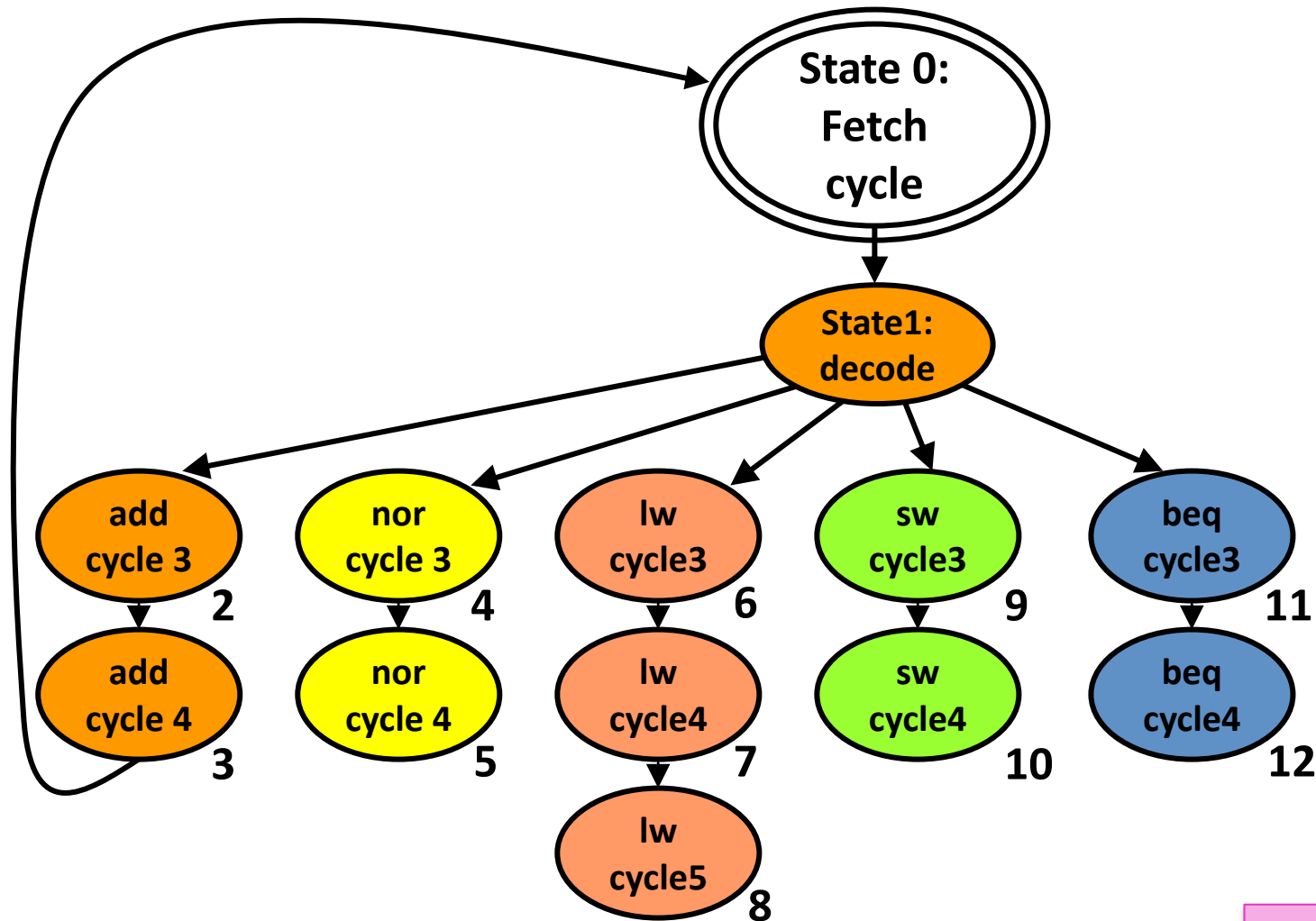
State machine for multi-cycle control signals (transition functions)




Note: we aren't worrying about JALR instruction in hardware going forward

Poll: How many bits of storage are needed to store the state?

Implementing FSM

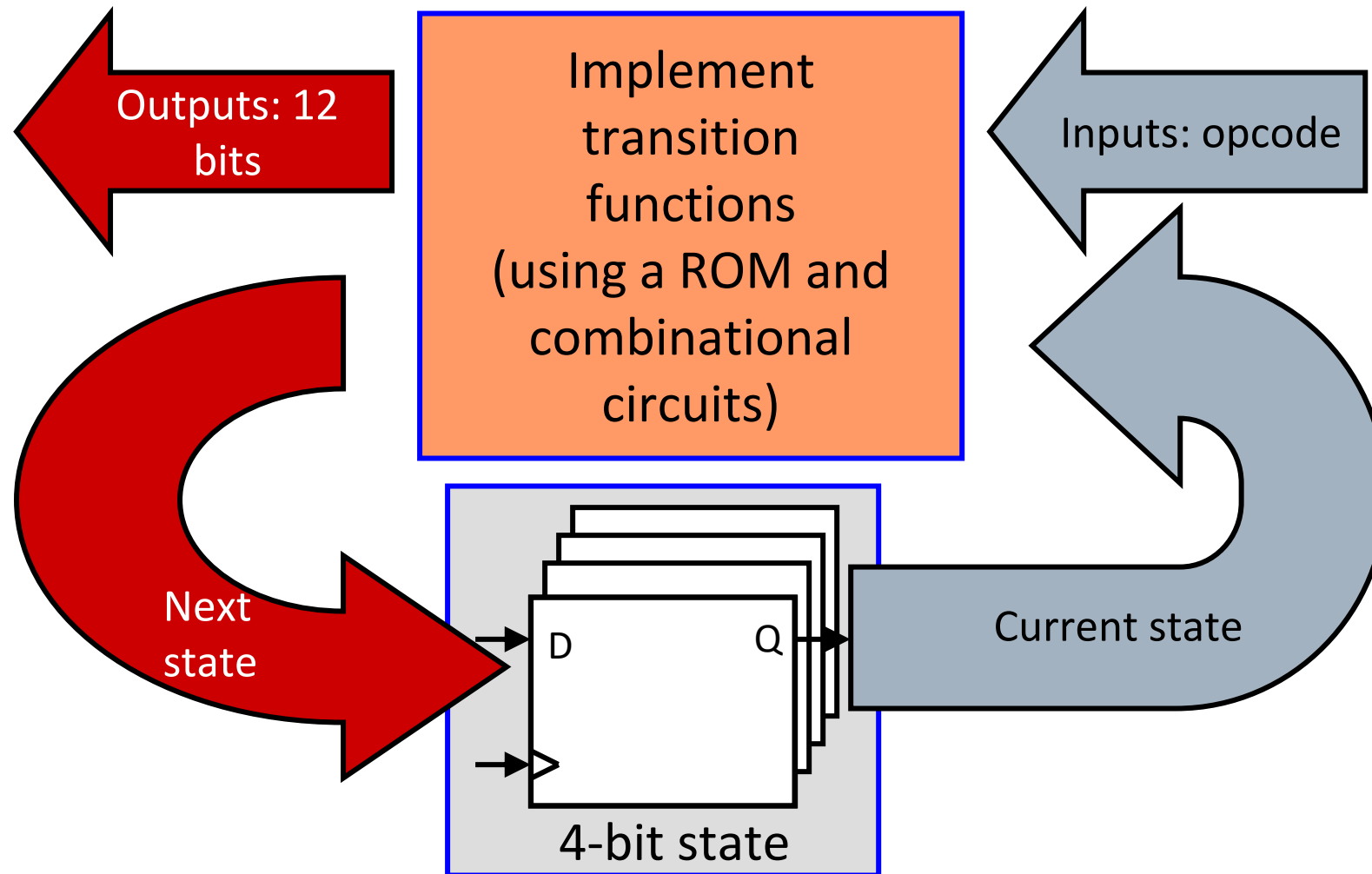

Building the Control ROM

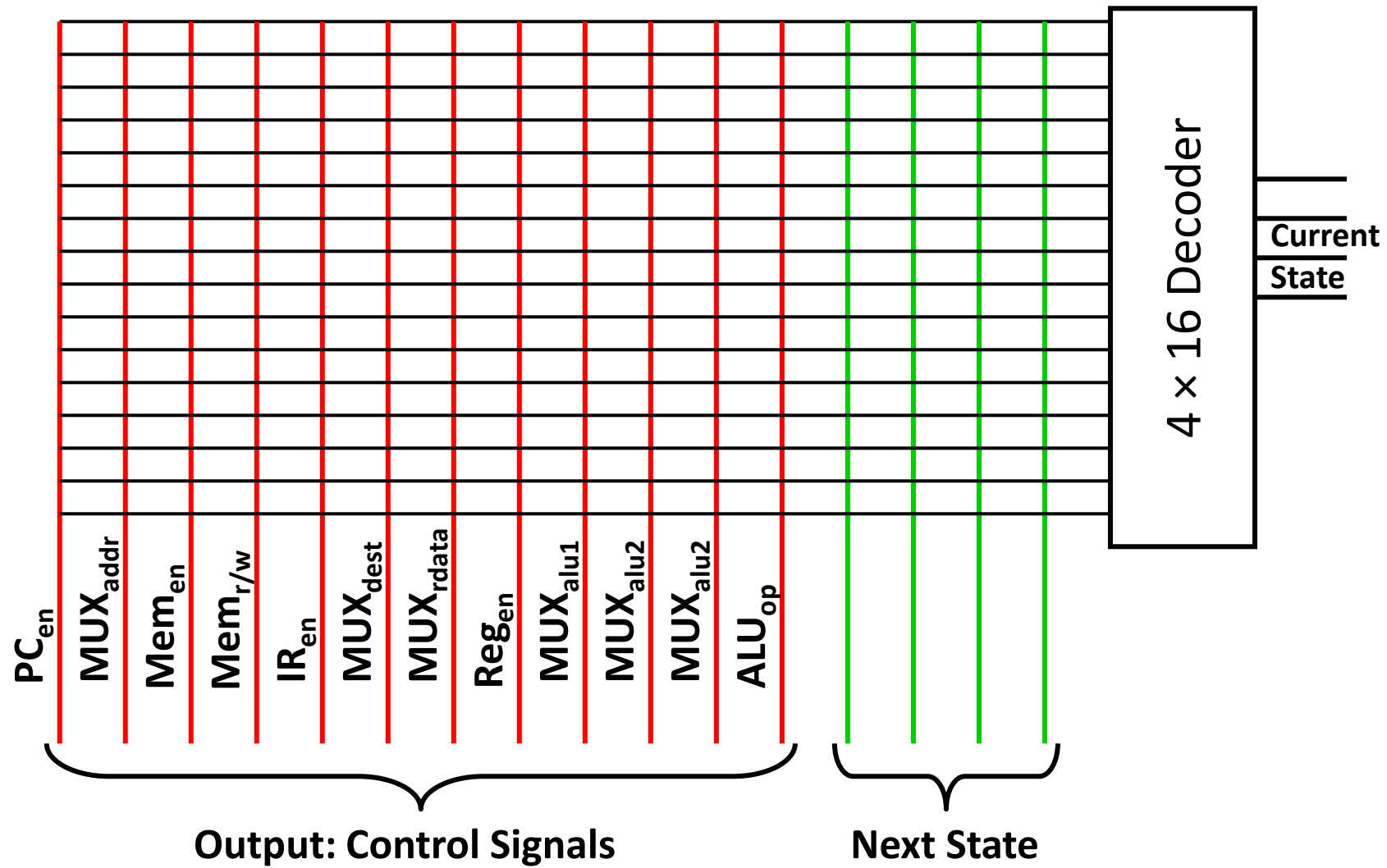


First Cycle (State 0) Fetch Instr

- What operations need to be done in the first cycle of executing any instruction?
 - Read memory[PC] and store into instruction register.
 - Must select PC in memory address MUX ($MUX_{addr} = 0$)
 - Enable memory operation ($Mem_{en} = 1$)
 - R/W should be (read) ($Mem_{r/w} = 0$)
 - Enable Instruction Register write ($IR_{en} = 1$)
 - Calculate PC + 1
 - Send PC to ALU ($MUX_{alu1} = 0$)
 - Send 1 to ALU ($MUX_{alu2} = 01$)
 - Select ALU add operation ($ALU_{op} = 0$)
 - $PC_{en} = 0$; $Reg_{en} = 0$; MUX_{dest} and $MUX_{rdata} = X$
- Next State: Decode Instruction


First Cycle (State 0) Fetch Instr

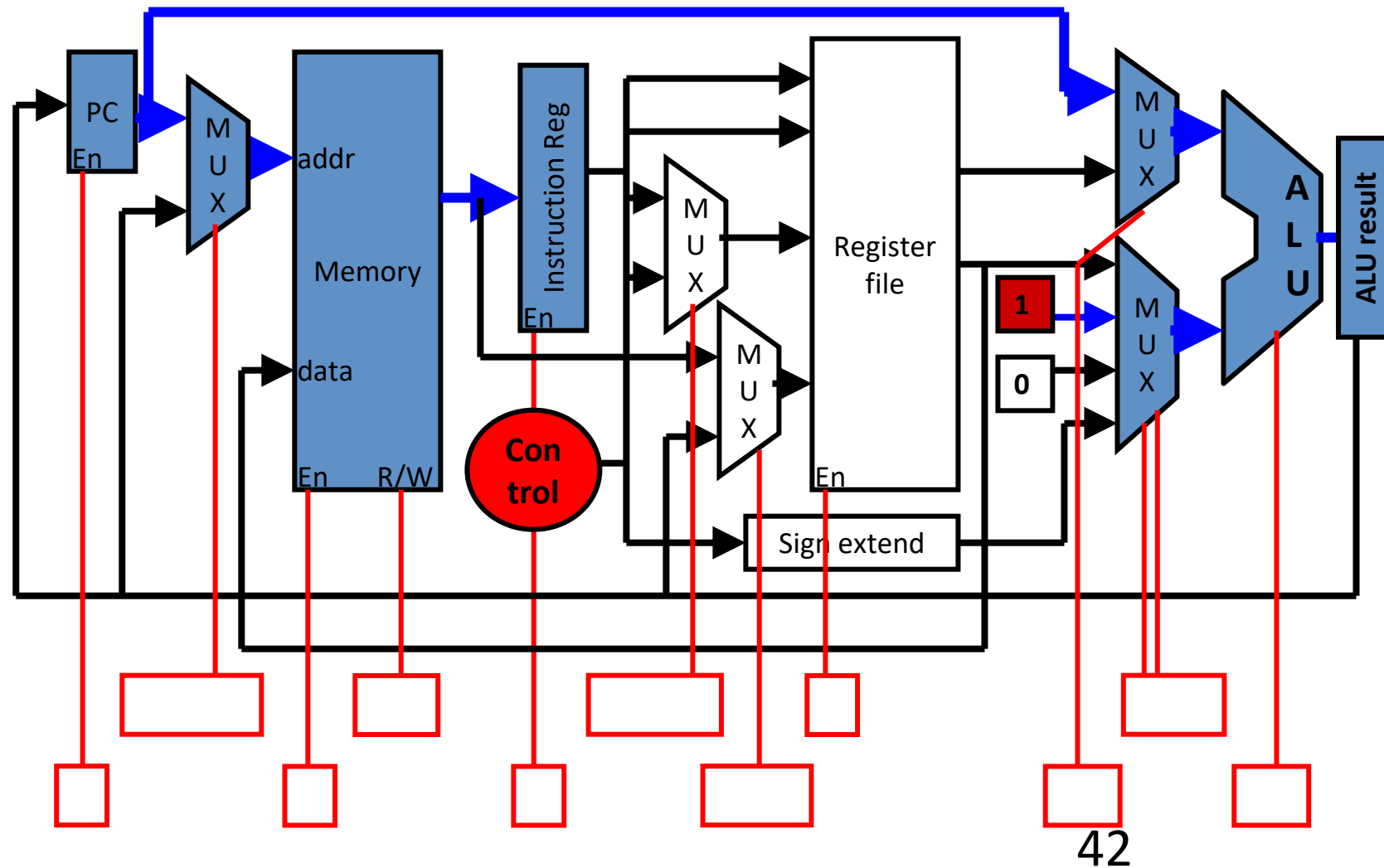This is the same for all instructions
(since we don't know the instruction yet!)




First Cycle (State 0) Fetch Instr

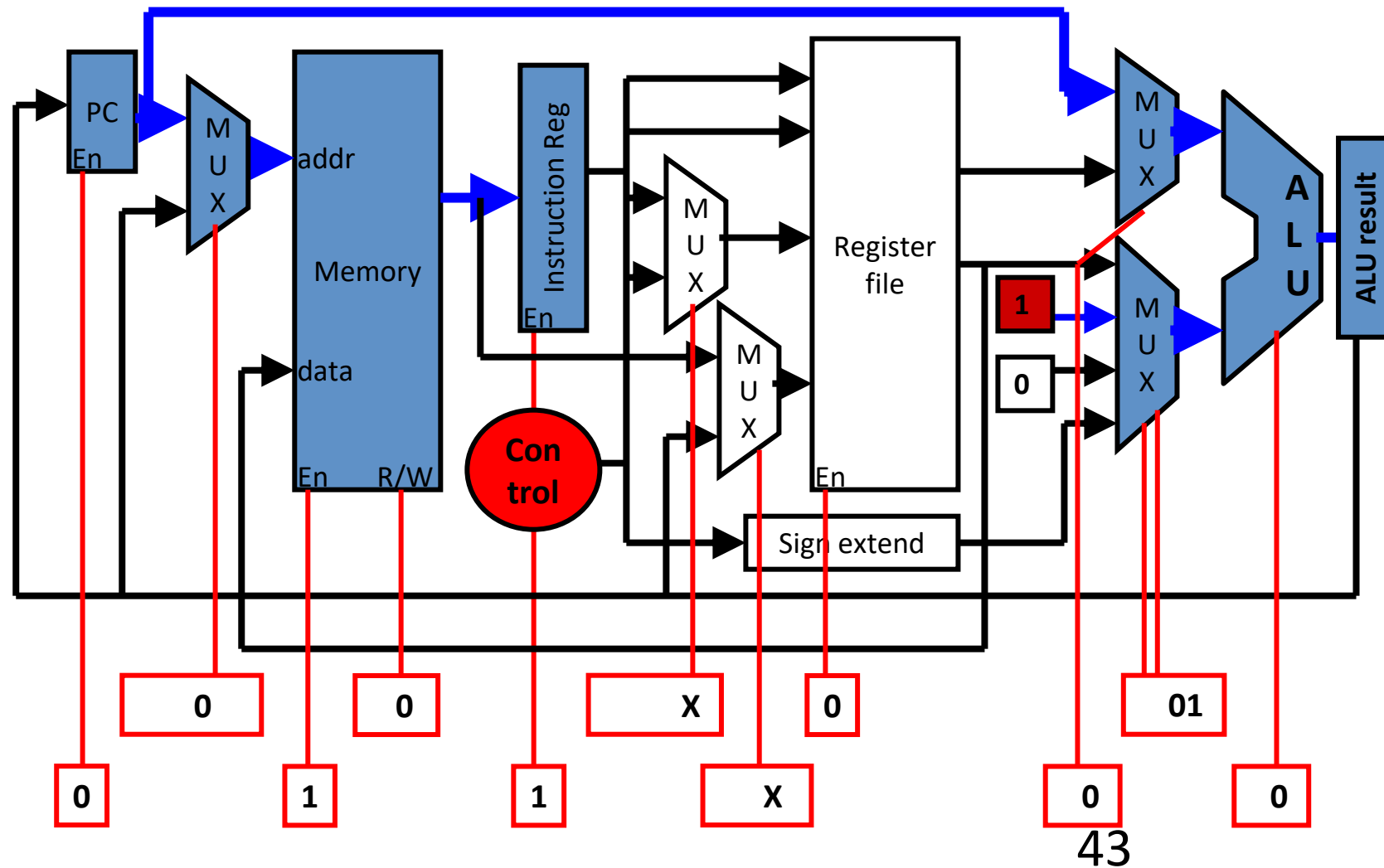This is the same for all instructions
(since we don't know the instruction yet!)



Building the Control ROM

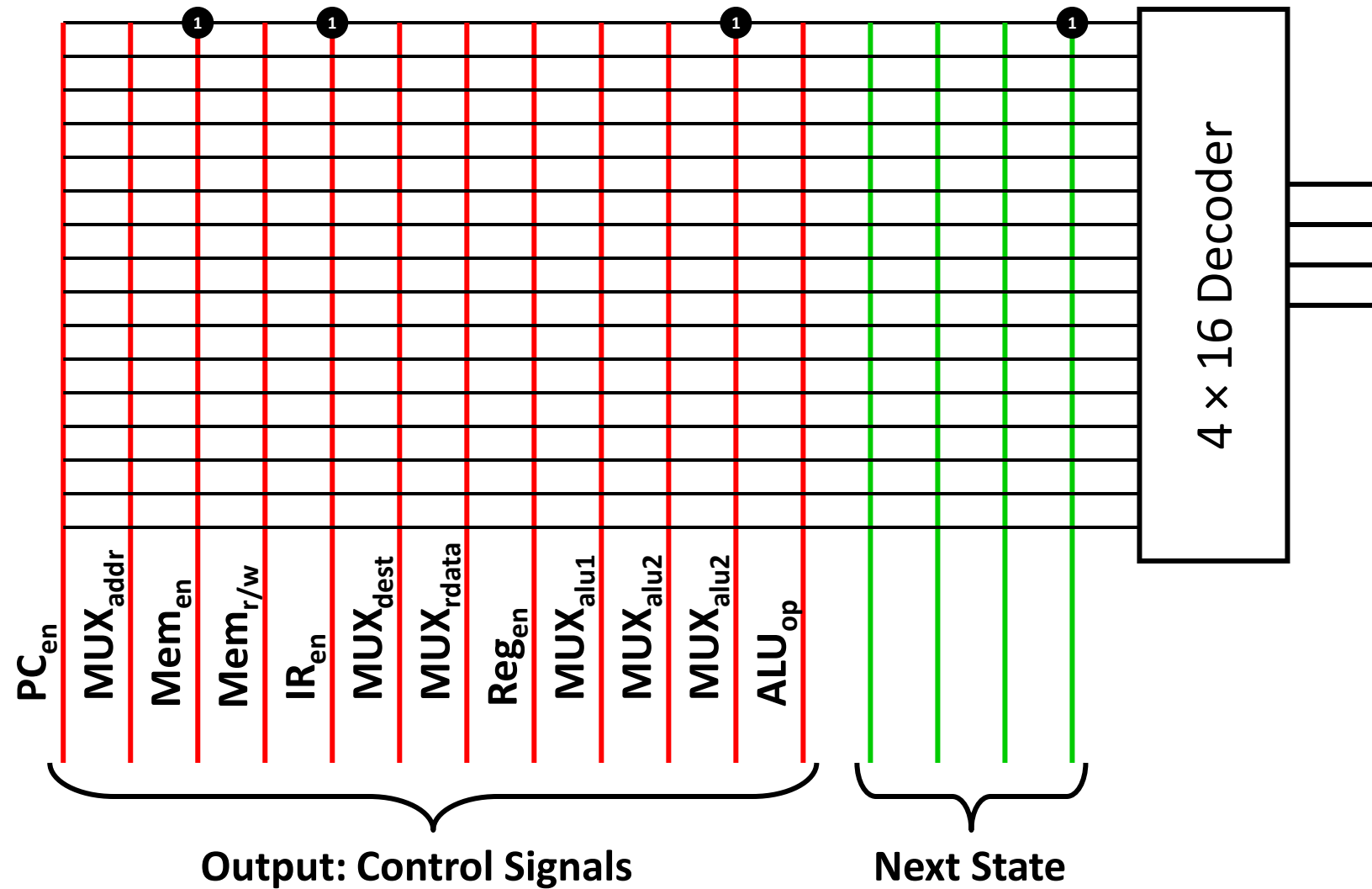

Next time

- Finish up multi-cycle processors
- Introduce pipelining